

JHARKHAND UNIVERSITY OF TECHNOLOGY

Diploma 3rd Semester Examination

ANALOG ELECTRONICS (ECE 301)

More Model Sets & Study Materials available here DiplomaWallah.in

Time: 3 Hours

Full Marks: 70

SET: 1

INSTRUCTIONS:

1. Question No. 1 is Compulsory.
2. Answer any **FOUR** questions from the remaining (Q.2 to Q.7).
3. Figures in the margin indicate full marks.

Q.1. Multiple Choice Questions

[2 × 7 = 14]

(i) The leakage current in a semiconductor is due to:

- | | |
|--------------------------|-----------------------|
| (a) Majority carriers | (b) Minority carriers |
| (c) Junction capacitance | (d) None of the above |

(ii) A Zener diode is mostly used as:

- | | |
|-------------------|-------------------------|
| (a) An amplifier | (b) A voltage regulator |
| (c) An oscillator | (d) A rectifier |

(iii) In a CE amplifier, the phase difference between input and output is:

- | | |
|----------|----------|
| (a) 0° | (b) 90° |
| (c) 180° | (d) 270° |

(iv) Ideally, the CMRR of an Op-Amp should be:

- | | |
|-----------|--------------|
| (a) Zero | (b) Infinity |
| (c) Unity | (d) 100 |

(v) Which oscillator is used for high-frequency applications?

- | | |
|------------------------|------------------------|
| (a) RC Phase Shift | (b) Wein Bridge |
| (c) Hartley Oscillator | (d) Crystal Oscillator |

(vi) Pin number 3 of IC 555 is used for:


- | | |
|-------------|---------------|
| (a) Trigger | (b) Reset |
| (c) Output | (d) Discharge |

(vii) The efficiency of a Class B push-pull amplifier is approximately:

- | | |
|-----------|----------|
| (a) 25% | (b) 50% |
| (c) 78.5% | (d) 100% |

Q.2. (a) Explain the working of **Class B Push-Pull Power Amplifier** with a neat circuit diagram.

[7]

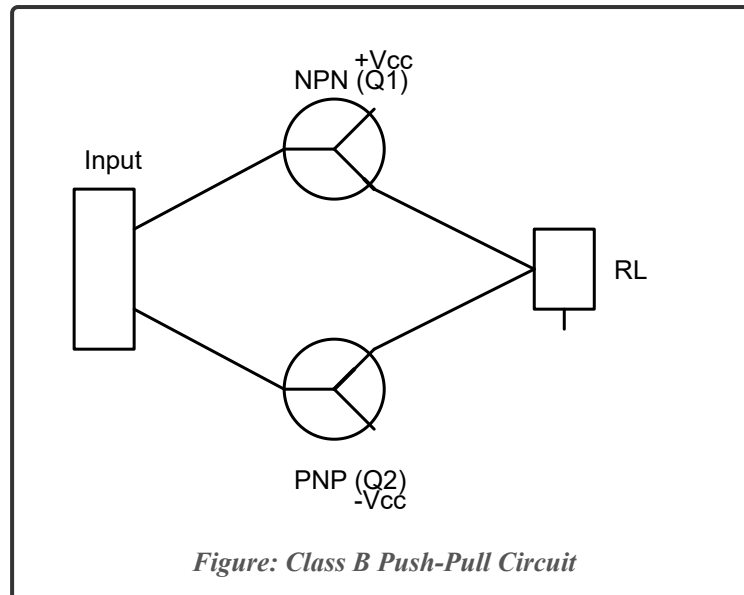


Q.2. (b) Derive the expression for the maximum conversion efficiency of a Class B amplifier.

[7]

Q.3. (a) Draw the circuit diagram of **RC Phase Shift Oscillator** using a BJT. Explain how phase shift is achieved.

[7]

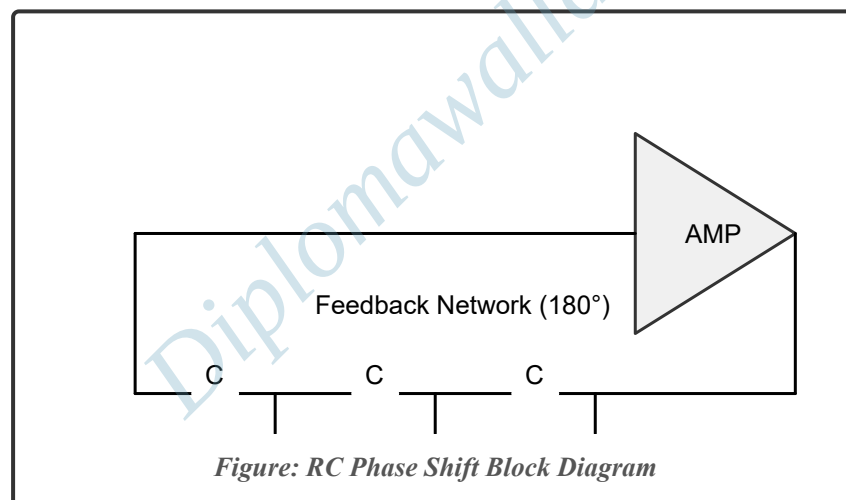


Q.3. (b) Determine the frequency of oscillation for an RC phase shift oscillator if $R = 10\text{k}\Omega$ and $C = 0.01\mu\text{F}$.

[7]


Q.4. (a) Explain the working of an Op-Amp as an **Integrator** with a circuit diagram.

[7]

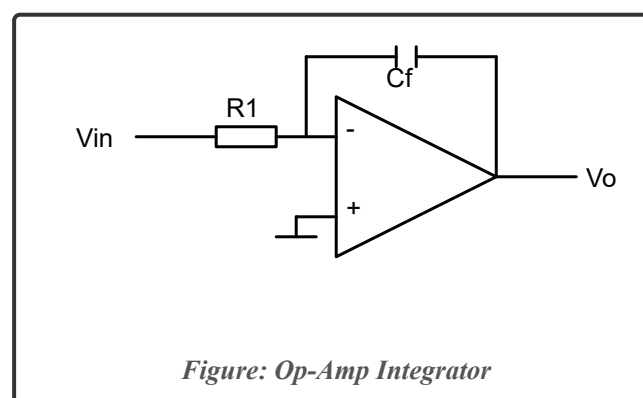


Q.4. (b) Draw the Functional Block Diagram of IC 555 Timer.

[7]

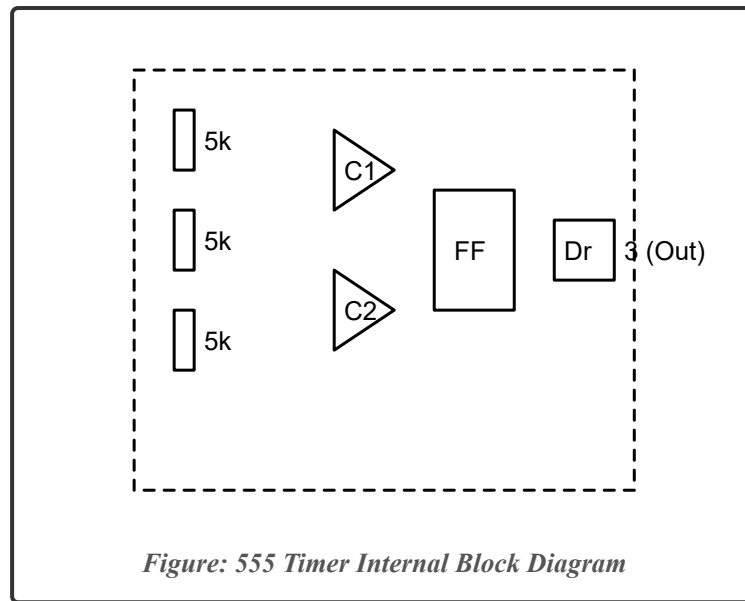


Q.5. (a) Draw the circuit diagram of a Voltage Divider Bias circuit.

[7]

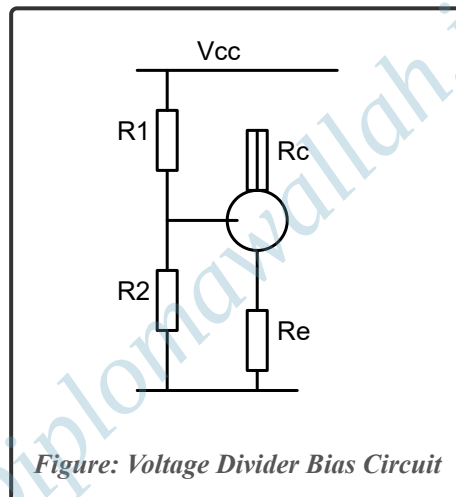

Q.5. (b) NUMERICAL: For the fixed bias circuit shown below, determine I_B and I_C .
 Given: $V_{cc} = 12V$, $R_b = 240k\Omega$, $R_c = 2.2k\Omega$, $\beta = 50$.

[7]

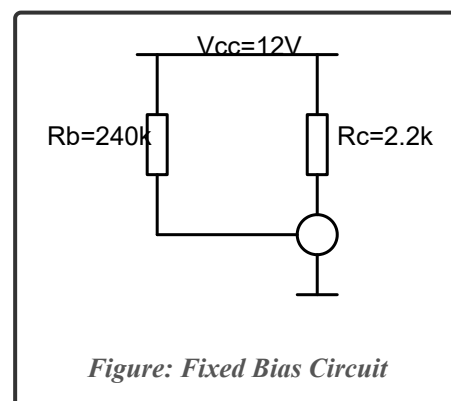

Q.6. Define Schmitt Trigger. Draw its circuit diagram using an Op-Amp and explain its working with the help of a Hysteresis Loop.

[14]

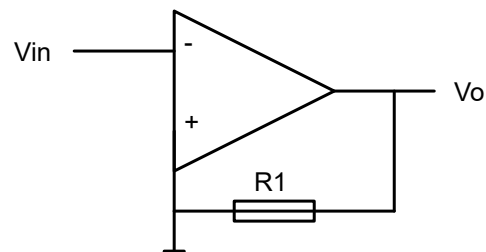


Figure: Schmitt Trigger Circuit

Q.7. Write Short Notes on (Any FOUR):

[3.5 × 4 = 14]

- SMPS (Switch Mode Power Supply)
- Barkhausen Criteria
- Active vs Passive Filters
- Zener Diode Characteristics
- Thermal Runaway

Diploma Wallah: Solutions Key

Q1 (MCQ Answers): (i) b, (ii) b, (iii) c, (iv) b, (v) c, (vi) c, (vii) c.

Q3(b) Numerical Hint:

Formula: $f = 1 / (2\pi RC\sqrt{6})$

Values: R=10k, C=0.01μF. Result ≈ **650 Hz**.

Q5(b) Numerical Hint:

Step 1: $I_B = (V_{cc} - 0.7) / R_b = (11.3 / 240k) = 47.08 \mu A$

Step 2: $I_C = \beta \times I_B = 50 \times 47.08 \mu A = 2.35 mA$.