

**JHARKHAND UNIVERSITY OF TECHNOLOGY**

**DIPLOMA 3RD SEMESTER EXAMINATION**

# **ANALOG ELECTRONICS (ECE 301)**

**DIPLOMA WALLAH**

**MORE MODEL SETS & STUDY MATERIALS AVAILABLE HERE**

**[DIPLOMAWALLAH.IN](http://DIPLOMAWALLAH.IN)**

---

**Time: 3 Hours**

**Full Marks: 70**

**SET: 3**

---

**INSTRUCTIONS:**

1. Question No. 1 is Compulsory.
2. Answer any **FOUR** questions from the remaining (Q.2 to Q.7).

## **Q.1. MULTIPLE CHOICE QUESTIONS**

**[2 × 7 = 14]**

**(i) A UJT is essentially a:**

(a) Current controlled device (b) Voltage controlled device  
(c) Relaxation Oscillator (d) All of the above

**(ii) The feedback fraction of Hartley Oscillator is decided by:**

(a) Capacitor divider (b) Inductor divider  
(c) Resistor divider (d) Transistor beta

**(iii) Op-Amp can be used as a summing amplifier in:**

(a) Inverting mode only (b) Non-inverting mode only  
(c) Both modes (d) Saturation mode

**(iv) Darlington Pair is used to achieve:**

(a) High Voltage Gain (b) High Current Gain  
(c) High Bandwidth (d) Low Input Impedance

**(v) Which class of amplifier conducts for less than 180 degrees?**

(a) Class A (b) Class B  
(c) Class C (d) Class AB

**(vi) A series voltage regulator uses a transistor in:**


(a) Series with Load (b) Parallel with Load  
(c) Feedback loop (d) None

**(vii) The maximum efficiency of a Centre-Tapped Full Wave Rectifier is:**

(a) 40.6% (b) 50%  
(c) 81.2% (d) 100%

## SECTION B (LONG ANSWER TYPE)


**Q.2. (a)** Explain the working of an **Op-Amp as a Summing Amplifier** (Adder) in inverting mode. Derive the expression:  $V_o = -(V_1 + V_2 + V_3)$ . [7]

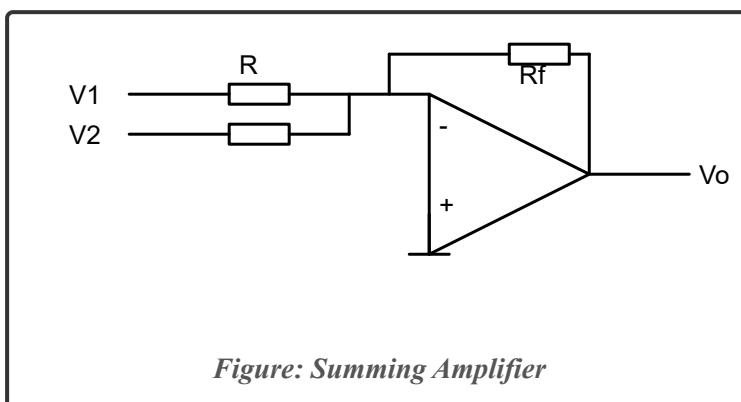

*Figure: Summing Amplifier*

**Q.2. (b)** Draw and explain the working of a **Centre-Tapped Full Wave Rectifier**. Calculate its Ripple Factor and Efficiency. [7]


**Q.3. (a)** Draw the circuit diagram of **Hartley Oscillator**. Explain its operation and write the formula for frequency of oscillation. [7]

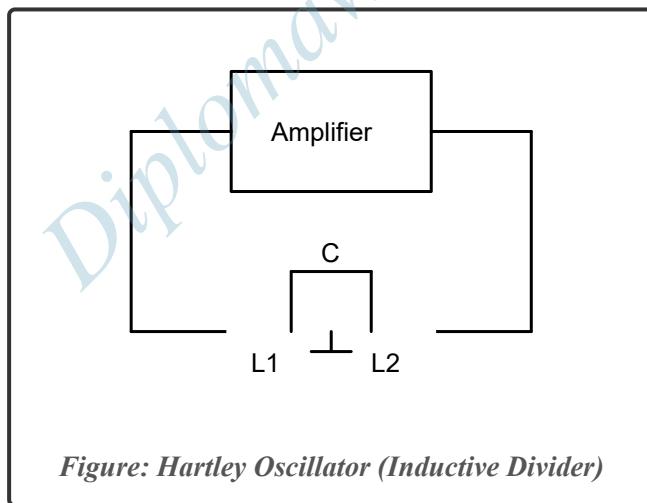

*Figure: Hartley Oscillator (Inductive Divider)*


**Q.3. (b)** Explain **Colpitts Oscillator**. How does it differ from Hartley Oscillator? (Hint: Uses Capacitive Divider). [7]

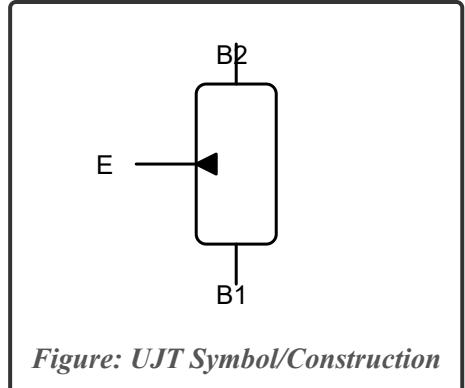**Q.4. (a)** Explain the construction and characteristics of **UJT (Uni-Junction Transistor)**. How is it used as a Relaxation Oscillator? [7]




**Q.4. (b)** Explain **Load Line Analysis** (DC Load Line). What is the significance of the Q-point in amplification? [7]

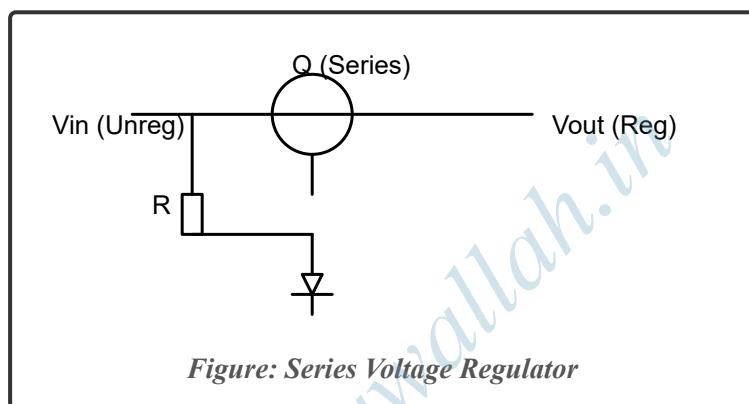**Q.5. (a)** Draw the circuit of a **Series Voltage Regulator** using a Transistor and Zener Diode. Explain its working. [7]



**Q.5. (b)** Explain **Voltage Doubler** circuit (Half Wave or Full Wave) with a neat diagram. [7]

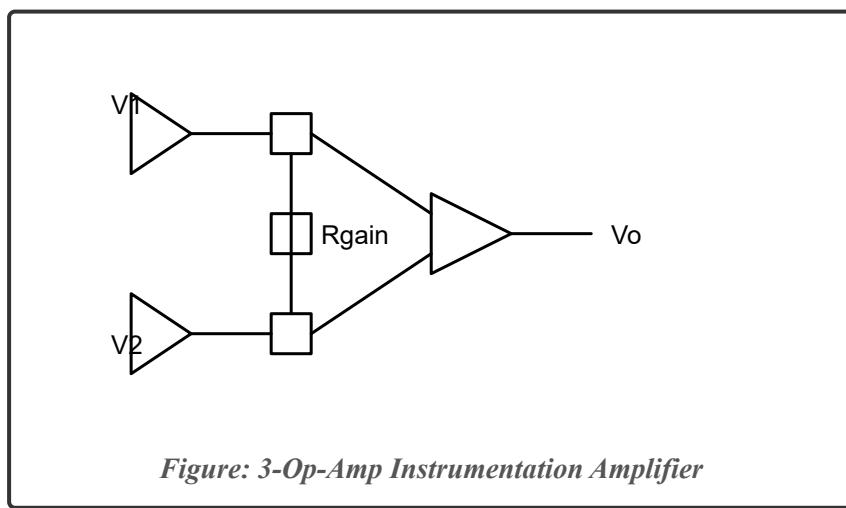**Q.6. [Long Answer]** Draw the circuit diagram of an **Instrumentation Amplifier** using 3 Op-Amps. Derive the expression for its output voltage. Why is it used in medical and industrial applications? [14]



**Q.7. WRITE SHORT NOTES ON (ANY FOUR):** [3.5 × 4 = 14]

a. Current Series Feedback

- b. Darlington Pair
- c. LED vs LCD
- d. Opto-Isolator
- e. Band Pass Filter

---

### SOLUTION KEY (PAPER 3)

**Q1 MCQ:** (i) b (Double base), (ii) b, (iii) a, (iv) b, (v) c, (vi) a, (vii) c.

**Q2(a) Hint:** Current at inverting node is sum of currents:  $I_1 + I_2 + I_3 = -I_f$ . Leads to  $V_o = -(V_1 + V_2 + V_3)$ .

**Q3(a) Hint:** Hartley uses two Inductors ( $L_1, L_2$ ) in series with parallel Capacitor.