

Unit :- 02

RESONANCE

Date :-


Page :-

* Resonance :-

(ii)

$$jX = -jX$$

Resonance is the phenomenon at which the response of the circuit is maximum at a given particular frequency.

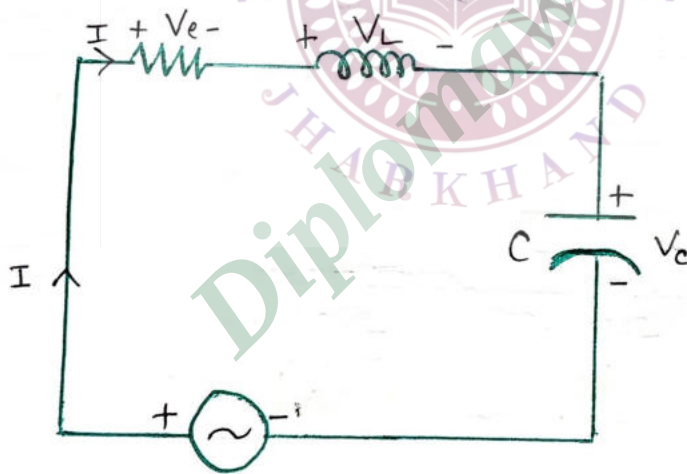* Series Resonance Circuit (RLC) :- $R \rightarrow$ Resistance $L \rightarrow$ Inductance $C \rightarrow$ Capacitor.

using KVL (Kirchhoff's voltage law),

$$-V + V_R + V_L + V_C = 0$$

$$V_R + V_L + V_C = V \quad \text{--- (1)}$$

$$V = IR + I(j\omega L) + I(-j\omega C)$$

$\downarrow$ Resistance $\downarrow$ Impedance $\downarrow$ Capacitor

$$V = I (R + jX_L - jX_C)$$

$$V = I (R + j(X_L - X_C))$$

→ Resonant Condition :-

when, $X_L - X_C = 0$

$$\boxed{X_L = X_C} \quad \text{---} \quad (ii)$$

At this time the phenomenon is called resonance. For maximum voltage across the capacitor or inductor, the condition is given by $X_L = X_C$.

$$V = IR + I(jX_L - jX_C)$$

$$V = IR + I(j(X_L - X_C))$$

$$\boxed{V = IR}$$

Here, $X_L = 2\pi fL$
 $X_C = \frac{1}{2\pi fC}$

$$X_L = X_C$$

$$\therefore 2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

$$f_r^2 = \frac{1}{(4\pi)^2 LC}$$

$$f_r = \sqrt{\frac{1}{4\pi^2 LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{CL}}$$

$$[f_r = f] \frac{V}{I} = I$$

$$(j\omega L - j\omega C) I + IR$$

Again, by using eqn (i) we get $\frac{V}{I} = I$

$$V = V_R + V_L + V_C$$

$$= IR + I(j\omega L) + I(-j\omega C) \quad \frac{V}{I} = I$$

$$= I(R + j\omega L - j\omega C)$$

$$= I(R + j(\omega L - \omega C))$$

$$V = IR$$

At resonance, the impedance of the circuit is minimum, hence the current is maximum. Here, $Z = (R + j(\omega L - \omega C))$

$$Z = \text{Impedance} \quad \frac{V}{I} = I$$

$$Z = R + j(\omega L - \omega C)$$

$$Z = R + j0$$

$$[\because \omega L = \omega C] \quad IR = IV$$

$$Z = R$$

$$\therefore V = IR$$

[from (iii)]

$$V = IR$$

Current :-

From eqn - (iii) $\frac{1}{\frac{1}{\omega L} - \frac{1}{\omega C}} = \omega Z$

$$I = \frac{V}{Z} \quad [Z = \omega Z]$$

$$I = \frac{V}{R + j(X_L - X_C)}$$

top eqn (i) now given pd, inopd
 $I = \frac{V}{R + jX_0}$ $[\because X_L = X_C]$

$$I = \frac{V}{R} \quad \text{Proved.}$$

* At resonance, the impedance of series RLC circuit reaches its minimum value. Hence, maximum current flow through this circuit at resonance.

i.e., $I = \frac{V}{Z}$

→ Voltage across resistor (V_R)

$$V_R = IR \quad [\because X_L = X_C]$$

$$V_R = \left(\frac{V}{R} \right) \times R \quad \left[\because I = \frac{V}{R} \right]$$

$$\boxed{V_R = V}$$

→ Voltage across Inductor :- (V_L)

$$V_L = I (j\omega L)$$

$$V_L = \frac{V}{R} (j\omega L)$$

$$V_L = j \left(\frac{\omega L}{R} \right) \cdot V$$

$$V_L = j Q V$$

Here, $Q = \frac{\omega L}{R}$
 $Q = \frac{V_L}{V} = \frac{|V_L|}{|V|}$

$$\therefore Q = \frac{X_L}{R}$$

$$\therefore |V_L| = |j Q V|$$

$$|V_L| = Q V$$

$$\cos \theta = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X_L^2}}$$

→ Voltage across Capacitor (V_C) :-

$$V_C = I (-j\omega C)$$

$$V_C = \left(\frac{V}{R} \right) (-j\omega C)$$

$$V_C = -j \left(\frac{\omega C}{R} \right) \cdot V$$

$$V_C = -j Q V$$

$$Q = \frac{X_C}{R}$$

$$(1) \cos^{-1} 0 = \theta$$

$$\theta = 90^\circ$$

$Q = \text{Quantity Factor}$
 Resistor
 Inductor
 Capacitor

$$|V_L| = |-jQV| = QV$$

* Series resonance RLC circuit is called as voltage magnification circuit because magnitude voltage across the inductor and capacitor is Q times the input sinusoidal voltage (V).

$$\text{i.e. } |V_L| = |V_C| = QV$$

Power Factor :-

$$\text{Power factor} = \cos \theta \quad \because |V \cos \theta| = |V| \quad \therefore [Z = R]$$

$$\cos \theta = \frac{R}{Z} = \frac{R}{R}$$

$$\therefore \cos \theta = 1$$

$$\theta = \cos^{-1}(1)$$

$$\boxed{\theta = 0^\circ}$$

Resistance $\rightarrow$ Same with current
Inductor $\rightarrow$ lead

Capacitor $\rightarrow$ lag.

* Phasor diagram of series Resonance RLC circuit :-

$$V = V_R + V_L + V_C$$

$$\bar{V} = \bar{V}_R + \bar{V}_L + (\bar{V}_C - j\bar{V}) + j\bar{V} = \bar{V}$$

[Phasor]

$$\bar{I} = \bar{I}_R + \bar{I} (j\bar{X}_L) + \bar{I} (-j\bar{X}_C) = \bar{V}$$

→ Phasor diagram :-


① Resistance :-



② Inductor :- ($\bar{V}_L$)



③ Capacitor :- ($\bar{V}_C$)

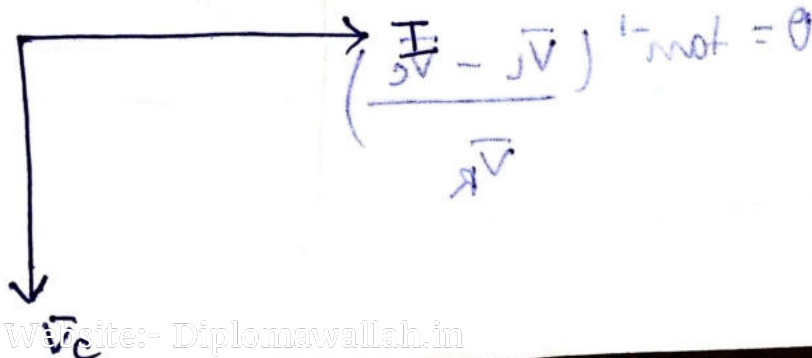

* Power factor Angle :-

$$\frac{\bar{V}_R - j\bar{V}}{j\bar{V}} = \frac{P}{Q} = \theta \text{ not}$$


$$\frac{\bar{I} - j\bar{V}}{j\bar{V}} \text{ not } = \theta$$

* For Voltage triangle phasor diagram
Assum ($V_L > V_C$)

Using Pythagoras theorem, $V^2 = V_R^2 + (V_L - V_C)^2$

$$\bar{V}^2 = \bar{V}_R^2 + (\bar{V}_L - \bar{V}_C)^2$$
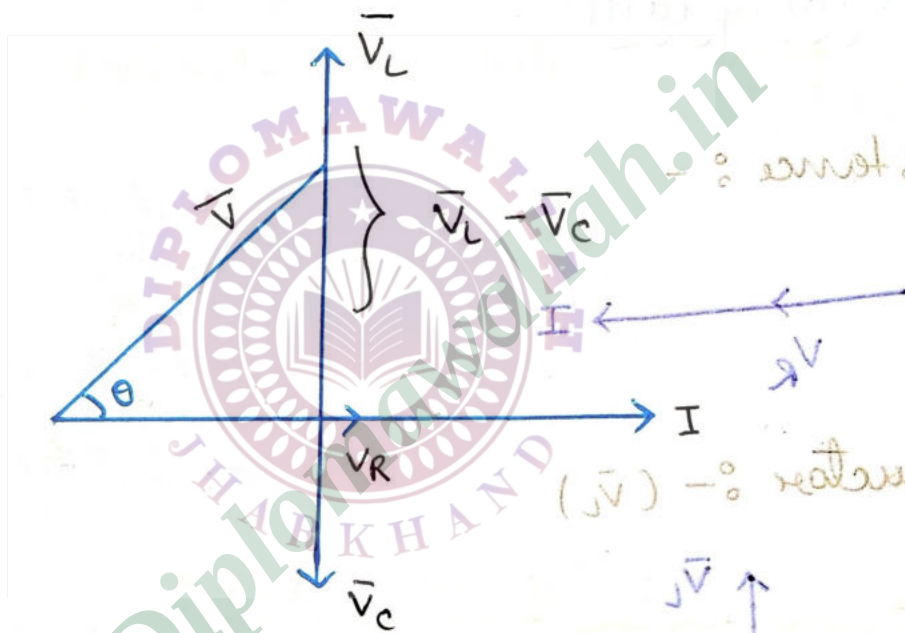
$$\bar{V} = \sqrt{\bar{V}_R^2 + (\bar{V}_L - \bar{V}_C)^2}$$



* Power factor Angle :-

$$\tan \theta = \frac{P}{b} = \frac{\bar{V}_L - \bar{V}_C}{\bar{V}_R}$$

$$\theta = \tan^{-1} \left(\frac{\bar{V}_L - \bar{V}_C}{\bar{V}_R} \right)$$

$$\cos \theta = \frac{b}{h} = \frac{\bar{V}_R}{\bar{V}}$$

$$\theta = \cos^{-1} \left(\frac{\bar{V}_R}{\bar{V}} \right)$$


$$\frac{\cos \theta - \cos \theta}{\theta} = \frac{1}{\theta} = \theta \text{ not}$$

For impedance triangle phasor diagram.

* Power factor angle :-

$$\tan \theta = \frac{p}{b} = \frac{\bar{x}_L - \bar{x}_C}{\bar{R}}$$
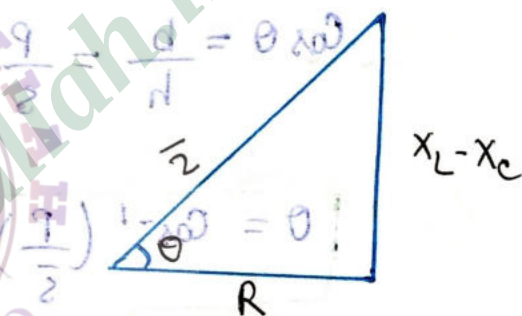
$$\theta = \tan^{-1} \left(\frac{\bar{x}_L - \bar{x}_C}{\bar{R}} \right)$$



* Power factor :-

$$\cos \theta = \frac{b}{h} = \frac{R}{Z}$$

$$\theta = \cos^{-1} \frac{R}{Z}$$

Impedance is minimum in resonance.

Current is maximum in resonance.


* Power Triangle:-

→ Power factor angle

$$\tan \theta = \frac{P}{b} = \frac{Q_L - Q_C}{P}$$

$$\theta = \tan^{-1} \left(\frac{Q_L - Q_C}{P} \right)$$
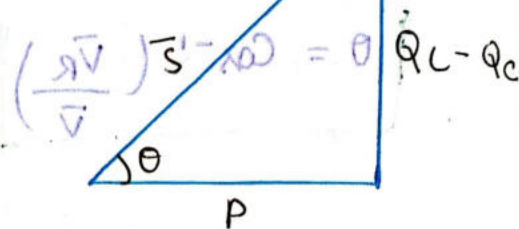
$$\frac{R\bar{V}}{\bar{V}} = \frac{d}{n} = \theta \text{ rad}$$



→ Power factor:-

$$\cos \theta = \frac{b}{h} = \frac{P}{S} = \frac{Q}{d} = \theta \text{ rad}$$

$$\theta = \cos^{-1} \left(\frac{P}{S} \right)$$

Characteristics of Series Resonance Circuit:-


- Resonance occurs when $X_L = X_C$. $\frac{R}{S} = \frac{d}{n} = \theta \text{ rad}$
- Resonant frequency $f_r = \frac{1}{2\pi\sqrt{LC}}$
- Impedance is minimum and the circuit is purely resistive.
- Current has a maximum value.

- When a number of frequencies are fed to it, it accept only one frequency i.e, resonant frequency (f_r) and reject all other frequencies.
- The current is maximum for this frequency and hence it is called acceptor circuit.

► Resonance Plot


→ Resonance plot for Inductor :-

Plot - 1

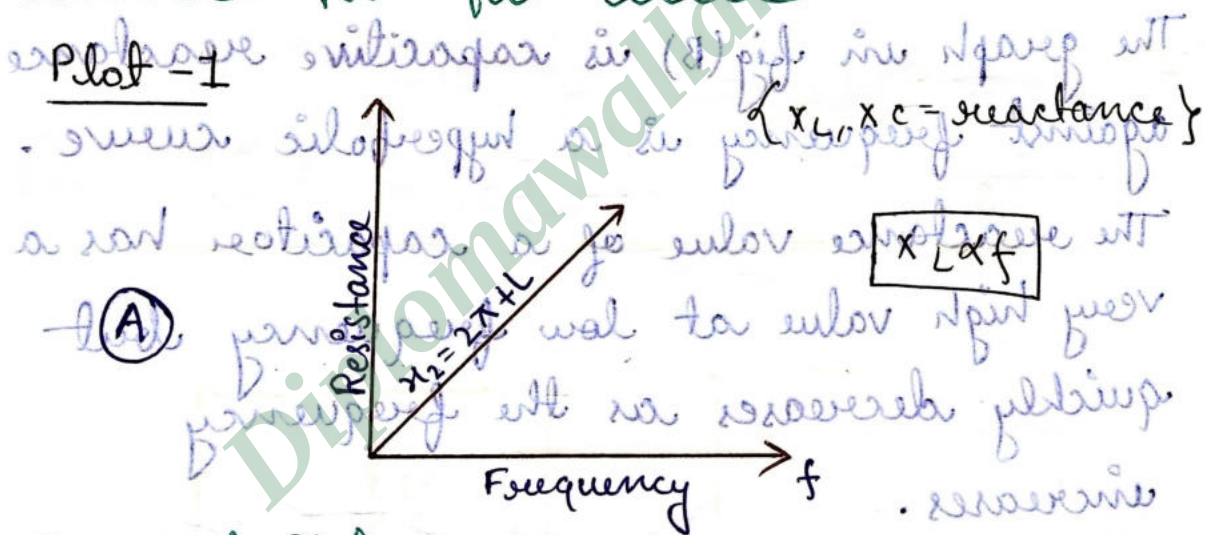

→ Resonant Plot for Capacitor :-

Plot - 2

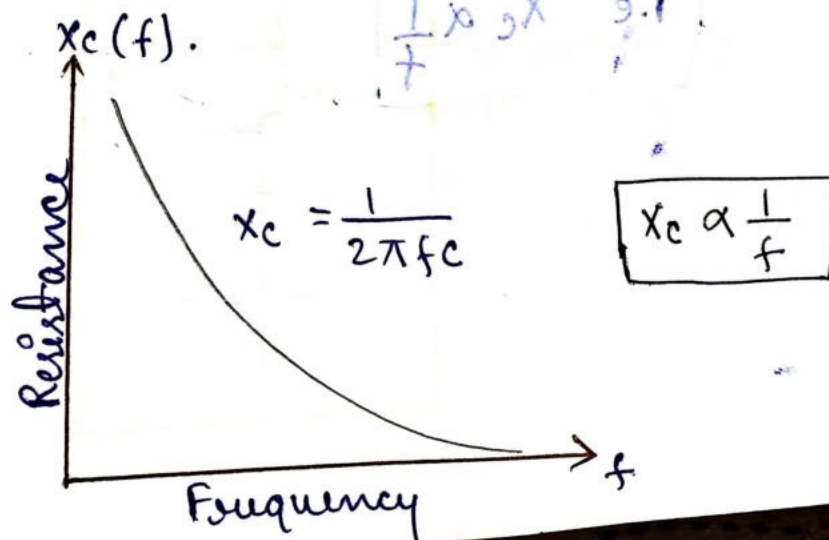

Plot : 1 :-

The graph in fig(A) is inductive reactance against frequency is a straight line linear curve. The inductive reactance value of an inductor increases linearly as the frequency increases.

i.e. $X_L \propto f$

Plot : 2 :-

The graph in fig(B) is capacitive reactance against frequency is a hyperbolic curve.

The reactance value of a capacitor has a very high value at low frequency but quickly decreases as the frequency increases.

i.e. $X_C \propto \frac{1}{f}$



$\frac{1}{f} \propto X$

$\frac{1}{2\pi f C} = X_C$

* See

Pa

Handwritten: KCL

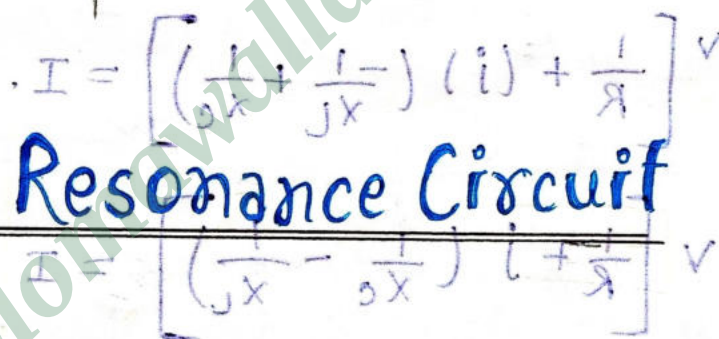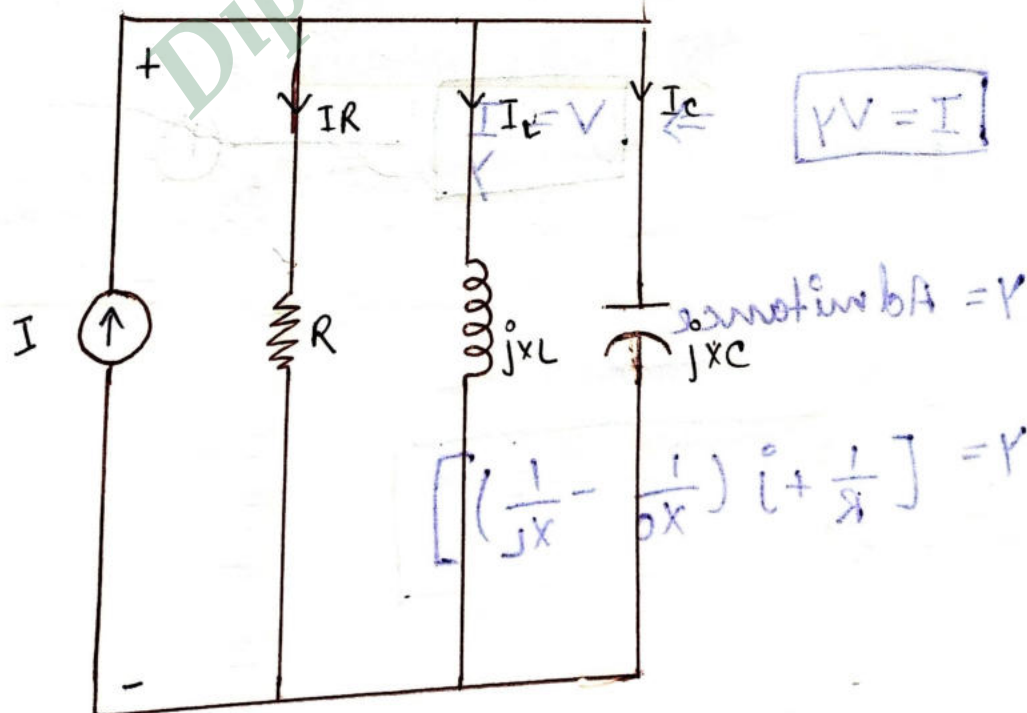
$$I = \left[\frac{1}{x} - \frac{1}{5x} \right] \left[+ \frac{1}{x} \right] \quad \checkmark$$


Using KCL,

$$-I + I_R + I_L + I_C = 0$$

$$-I + \frac{V}{R} + \frac{V}{jX_L} + \frac{V}{-jX_C} = 0$$

$$\frac{V}{R} + \frac{V}{jX_L} + \frac{V}{-jX_C} = I$$

$$\frac{V}{R} + \frac{(-jV)}{X_L} + \frac{(jV)}{X_C} = I$$

$$V \left(\frac{1}{R} + \frac{(-j)}{X_L} + \frac{j}{X_C} \right) = I$$

$$V \left[\frac{1}{R} + (j) \left(-\frac{1}{X_L} + \frac{1}{X_C} \right) \right] = I$$

$$V \left[\frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right) \right] = I$$


$$I = VY$$

$$\Rightarrow$$

$$V = \frac{I}{Y}$$

$Y = \text{Admittance}$
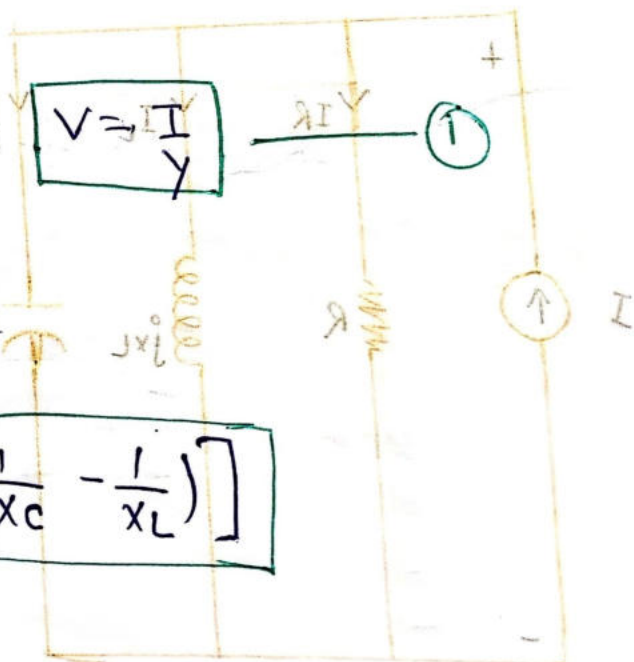
$$Y = \left[\frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right) \right]$$



→ ∴ The admittance 'Y' of the parallel RLC circuit will be

$$Y = \frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right)$$

→ In Parallel RLC circuit resonance occurs when imaginary term of admittance, 'Y', is 0.

i.e the value of $\frac{1}{X_C} - \frac{1}{X_L} = 0$

$$\frac{1}{X_C} = \frac{1}{X_L}$$

$$X_L = X_C$$

The above resonance condition is same as that of series RLC circuit. So, the resonance frequency, f_r will be same in both series RLC circuit and parallel RLC circuit.

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$0 = \frac{1}{X_C} - \frac{1}{X_L}$$

$$\left[\frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right) \right] V = I$$

$$\frac{V}{R} = I$$

$$V = IR$$

* Admittance :- The admittance of a circuit will be the reciprocal of its impedance.

$$Y = \frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right)$$

Now, $X_L = X_C$

$$Y = \frac{1}{R} + j(0)$$

$$Y = \frac{1}{R}$$

∴ The admittance 'Y' of parallel RLC circuit is equal to the reciprocal of resistor 'R'.

$$X_C = -jX_L$$

$$\text{i.e. } Y = \frac{1}{R}$$

* Voltage :- The voltage across each element in a parallel RLC circuit is the same as the voltage across the entire circuit.

$$\frac{1}{X_C} - \frac{1}{X_L} = 0$$

$$I = V \left[\frac{1}{R} + j(0) \right]$$

$$I = \frac{V}{R}$$

$$V = IR$$

$\therefore$ Voltage across all the element of parallel RLC circuit at resonance $V = IR$

The admittance of Parallel RLC circuit reaches to minimum value hence, maximum voltage is present across each element of this circuit at resonance.

$$\uparrow \boxed{V = \frac{I}{Y}} \downarrow$$

$$[\text{from (ii)}] = |jI|$$

* Current flowing through Resistor $\therefore (I_R)$

$$I_R = \frac{V}{R}$$

$$\frac{V}{j\omega L} = jI$$

$$I_R = \frac{IR}{R}$$

{ using Ohm's law }

$$\boxed{I_R = I}$$

$$I \left(\frac{R}{j\omega L} \right) = jI$$

$\therefore$ Current flowing through resistor at resonance

$$|I_R| = |jI|$$

$$\boxed{I_R = I}$$

$$\frac{R}{j\omega L} = j$$

* Current flowing through Inductor

$$I_L = \frac{V}{j\omega L}$$

$$\boxed{|I_L| = |jI|}$$

$$I_L = \frac{IR}{j\omega L}$$

bellareg to tunnel at the same point. $\therefore$

$$I_L = \frac{-jIR}{X_L}$$

increase. $I_L = -j \left(\frac{R}{X_L} \right) \times I$

follow minimum, same value minimum at
 tunnel at the point where the current is
 maximum to

$$I_L = -jQI$$

$$Q = \frac{R}{X_L}$$

$Q = \text{quality factor.}$

Magnitude

$$|I_L| = |QI|$$

$$\frac{I}{Y} = V$$

* Current flowing through Capacitor:-

$$I_C = \frac{V}{-jX_C}$$

$$\frac{V}{R} = IR$$

$$I_C = j \frac{IR}{X_C}$$

$$\frac{IR}{R} = IR$$

$$I_C = j \left(\frac{R}{X_C} \right) I$$

$$I = IR$$

to solve the problem. $I_C = jQI$

$$I_C = jQI$$

$Q = \text{Quality Factor}$

$$Q = \frac{R}{X_C}$$

$$I = \frac{Q}{X_C} I$$

$$|I_C| = |QI|$$

Magnitude


$$\frac{IR}{jX_C} = jI$$

∴ Parallel resonance RLC circuit is called as current magnification circuit because magnitude of the current flowing through inductor and capacitance is equal to Q the input sinusoidal current 'I'.

Date: 09.12.24

Day: Monday

Phasor Diagram

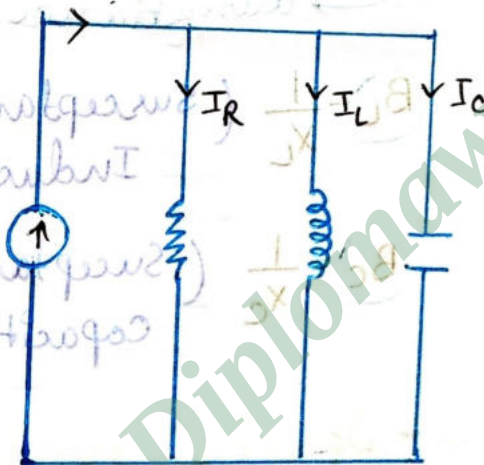

$$\bar{I} = \bar{I}_R + \bar{I}_L + \bar{I}_C$$

$$\frac{\bar{V}}{\bar{Z}} = \frac{V}{R} + \frac{V}{jX_L} + \frac{V}{-jX_C}$$

$$\frac{\bar{V}}{\bar{Z}} = \bar{V} \left(\frac{1}{R} + \frac{1}{jX_L} + \frac{1}{-jX_C} \right)$$

$$\frac{1}{\bar{Z}} = \left(\frac{1}{R} + \frac{1}{jX_L} - \frac{1}{jX_C} \right)$$

$\frac{1}{Z} = \left(\frac{1}{R} - j \frac{1}{X_L} + \frac{j}{X_C} \right)$ is an admittance called $\therefore$
 admittance is the reciprocal of impedance
 $\frac{1}{Z} = \left(\frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right) \right)$ is called admittance
 admittance has two components: conductance (real part) and susceptance (imaginary part)
 $Y = \{ G + j(B_C - B_L) \}$ is admittance at θ at large is

R = Resistance

G = Conductance

Y = Admittance

Z = Impedance

L = Inductance

C = Capacitance.


$G = \frac{1}{R}$ (Reciprocal of Resistance)
 $\rightarrow$ Conductance

$Y = \frac{1}{Z}$ (Reciprocal of Impedance)
 $\rightarrow$ admittance.

$B_L = \frac{1}{X_L}$ (Susceptance of Inductor)

$B_C = \frac{1}{X_C}$ (Susceptance of Capacitor)

★ Current Triangle :-

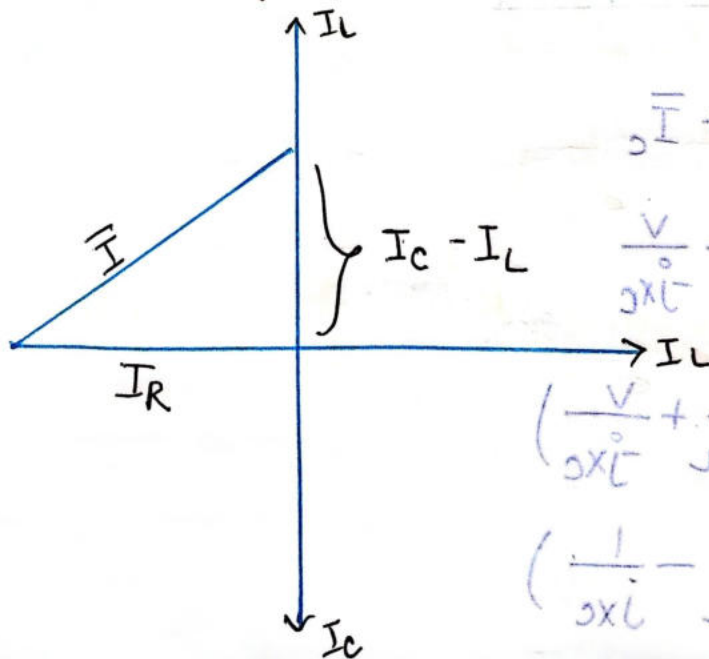

$$\bar{I} = \bar{I}_R + j\bar{I}_L + j\bar{I}_C = \bar{I}$$

$$\frac{V}{R} + \frac{V}{jX_L} + \frac{V}{-jX_C} = \frac{V}{Z}$$

$$\left(\frac{V}{R} - \frac{j}{X_L} + \frac{j}{X_C} \right) \bar{V} = \frac{\bar{V}}{Z}$$

$$\left(\frac{1}{R} - \frac{j}{X_L} + \frac{j}{X_C} \right) = \frac{1}{Z}$$

By using Pythagoras Theorem

$$h^2 = p^2 + b^2$$

$$\bar{I}^2 = \bar{I}_R^2 + (\bar{I}_C - \bar{I}_L)^2 (1 - \cos \theta) + \bar{I}_R \cos \theta = \bar{I}^2$$

$$\bar{I} = \sqrt{\bar{I}_R^2 + (\bar{I}_C - \bar{I}_L)^2 (1 - \cos \theta) + \bar{I}_R \cos \theta} = \bar{I}$$


* Power factor angle $\tan \theta = \frac{P}{b} = \frac{\bar{I}_C - \bar{I}_L}{\bar{I}_R}$

$$\theta = \tan^{-1} \left(\frac{\bar{I}_C - \bar{I}_L}{\bar{I}_R} \right)$$

* Power factor $\cos \theta = \frac{b}{h} = \frac{\bar{I}_R}{\bar{I}}$

$$\theta = \cos^{-1} \left(\frac{\bar{I}_R}{\bar{I}} \right)$$

Admittance triangle

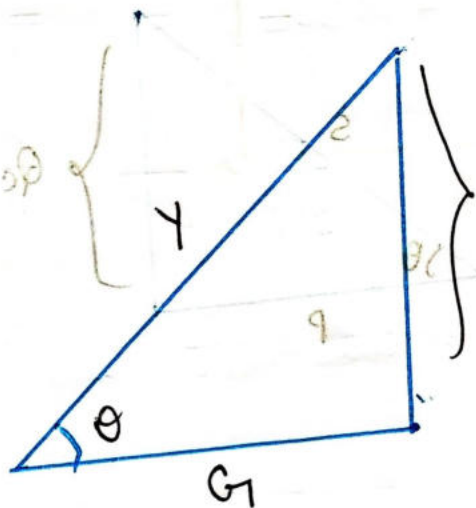

$$Y = \sqrt{G^2 + (B_C - B_L)^2}$$

$$Y = \sqrt{G^2 + (B_C - B_L)^2}$$

By using Pythagoras Theorem :-

$$h^2 = p^2 + b^2$$

$$\bar{Y}^2 = G^2 + (B_C - B_L)^2 \left(\frac{\bar{I} - \bar{I}}{\bar{I}} \right) + \frac{B_C - B_L}{G} \bar{I} = \bar{I}$$

$$\bar{Y} = \sqrt{G^2 + (B_C - B_L)^2 \left(\frac{\bar{I} - \bar{I}}{\bar{I}} \right) + \frac{B_C - B_L}{G} \bar{I}} = \bar{I}$$

* Power factor angle $\tan \theta = \frac{p}{b} = \frac{B_C - B_L}{G}$

$$\theta = \tan^{-1} \left(\frac{B_C - B_L}{G} \right)$$

* Power factor $\cos \theta = \frac{p}{h} = \frac{G}{Y}$

$$\theta = \cos^{-1} \left(\frac{G}{Y} \right)$$


Power triangle :-

By using Pythagoras Theorem :-

$$h^2 = p^2 + b^2$$

$$S^2 = P^2 + (Q_C - Q_L)^2$$

$$\bar{S} = \sqrt{P^2 + (Q_C - Q_L)^2}$$

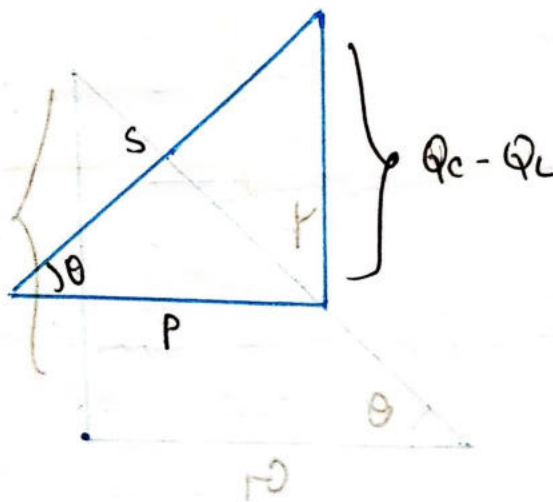


* Power factor angle $\tan \theta = \frac{P}{b} = \frac{Q_C - Q_L}{P}$

$$\theta = \tan^{-1} \left(\frac{Q_C - Q_L}{P} \right)$$

* Power factor $\cos \theta = \frac{b}{h} = \frac{P}{S}$


$$\theta = \cos^{-1} \left(\frac{P}{S} \right)$$

▷ Resonance Plot

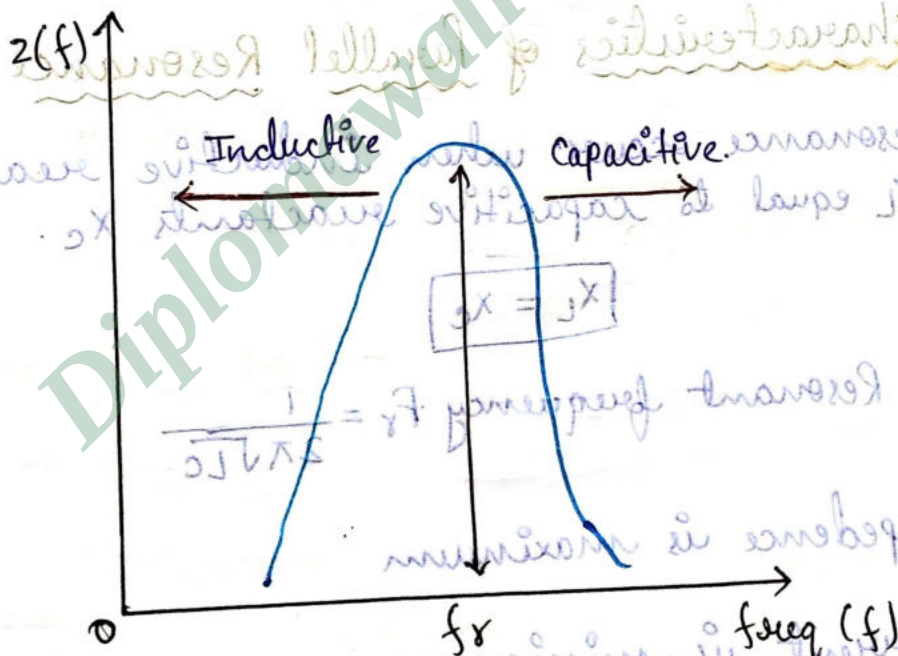

The circuit is called a series resonant circuit. It is called a series resonant circuit because it is in series with the load. Hence, it is called a series resonant circuit.

Surceptance at Resonance

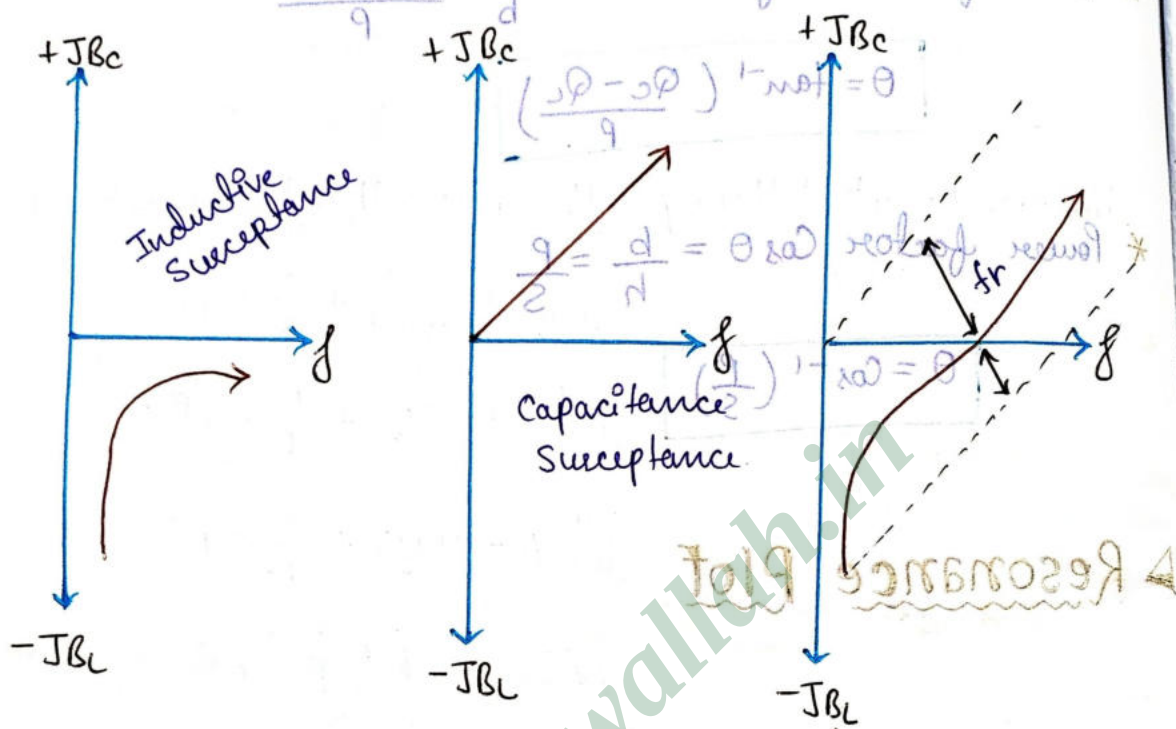

Characteristics of Parallel Resonance

- 1) Resonance occurs when inductive reactance X_L equal to capacitive reactance X_C .

$$X_L = X_C$$

$$\text{Resonant frequency } F_r = \frac{1}{2\pi\sqrt{LC}}$$

- 2) Impedance is maximum.

- 3) Current is minimum.

- 4) The circuit rejects F_r but allows the current to flow for other frequencies. Hence, it is called a rejector circuit.

* Condition for resonance parallel RLC circuit :-

- In parallel resonance circuit the condition for resonance occurs when the reactive power of the capacitor cancel each other out.

- This typically happens at a specific frequency known as resonant frequency.

* Condition :-

$$\frac{1}{j\omega L} + j\omega C + \frac{1}{R} = \frac{1}{R}$$

There are two types of condition :-

① Impedance condition :-

The total impedance of the circuit becomes purely resistive at resonant frequency.

② Frequency Condition :-

$$\frac{1}{j\omega} = j\omega$$

The resonant frequency can be calculated using the formula $f_r = \frac{1}{2\pi\sqrt{LC}}$

where as L is the inductance in henries & C is the capacitance in Farad.

$$\frac{1}{j\omega L} = j\omega C$$

$$j\omega C = \omega$$

$$\frac{1}{\omega L} = \omega$$

$$\frac{1}{\omega L} = j\omega C$$

$$\frac{1}{\omega^2 L C} = 1$$

Date: 13.12.24 Day: Friday

Expression for resonant frequency for Parallel RLC circuit

The total admittance of the parallel tuned circuit.

$$Y_T = \frac{1}{R} + \frac{1}{j\omega C} + \frac{1}{j\omega L}$$

$$Y_T = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$Y_T = \frac{1}{R} + j\omega C - j\frac{1}{\omega L}$$

$$Y_T = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

At resonant condition the imaginary part becomes zero.

$$\therefore \omega C = \frac{1}{\omega L}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega = 2\pi f$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\begin{cases} \omega = 2\pi f \\ \text{angular frequency} \end{cases}$$

Series Resonance

$$\frac{V}{R} = I \quad \text{pd}$$

Condition for RLC series circuit :-


i) Inductive reactants should be equal to capacitive reactants.

$$X_L = X_C$$


ii) The power factor $\cos \phi$ is equal to 1. where $\phi = 0$

$$\cos \phi = 1$$


$$\phi = 0^\circ$$

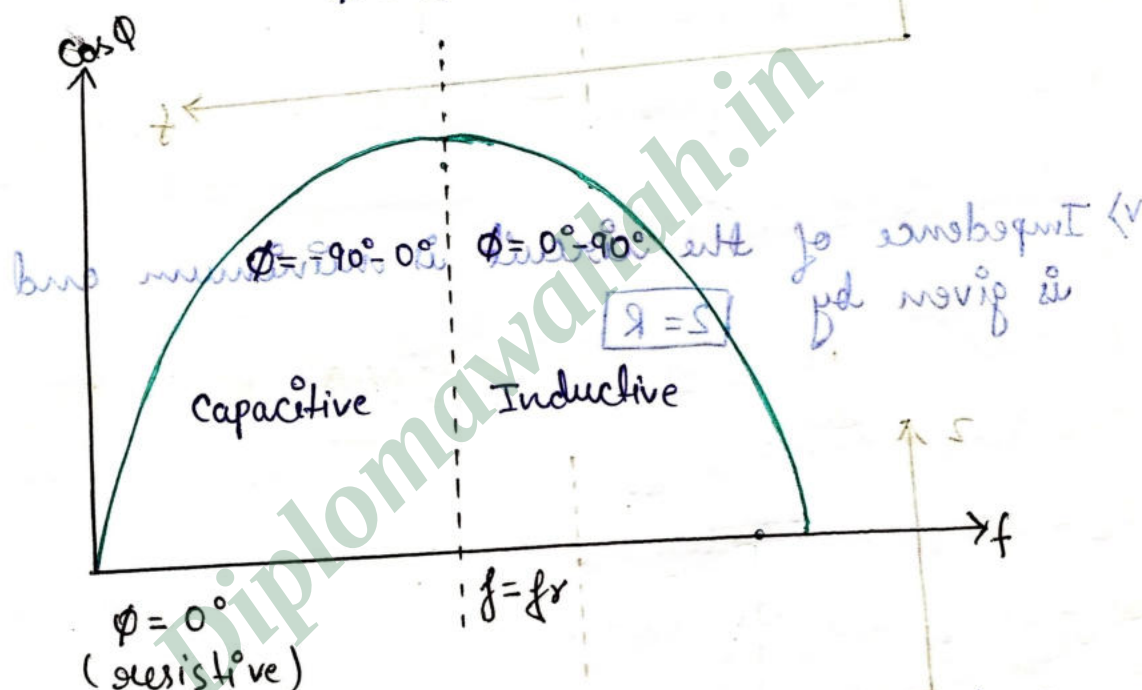

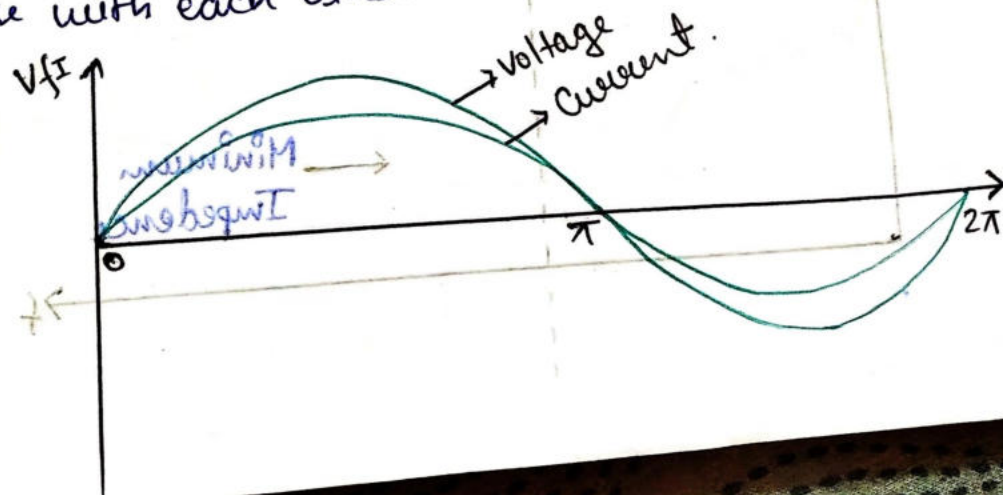
iii) The voltage and current in the RLC circuit are in phase with each other.



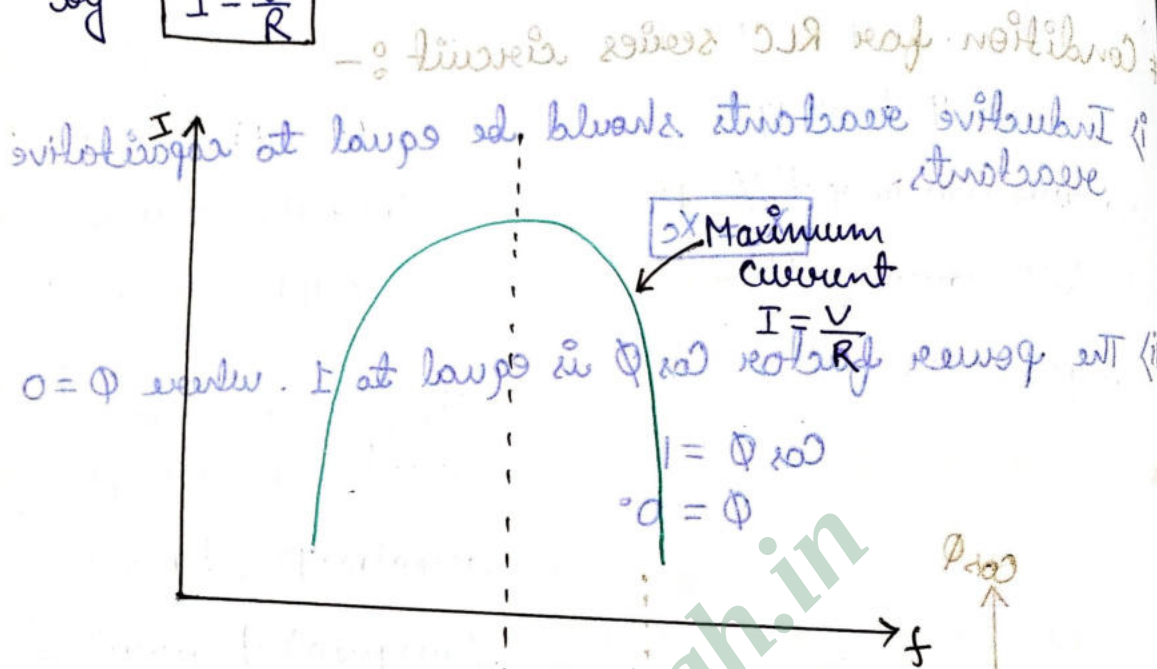iv) Current in the circuit is maximum and given by $I = \frac{V}{R}$



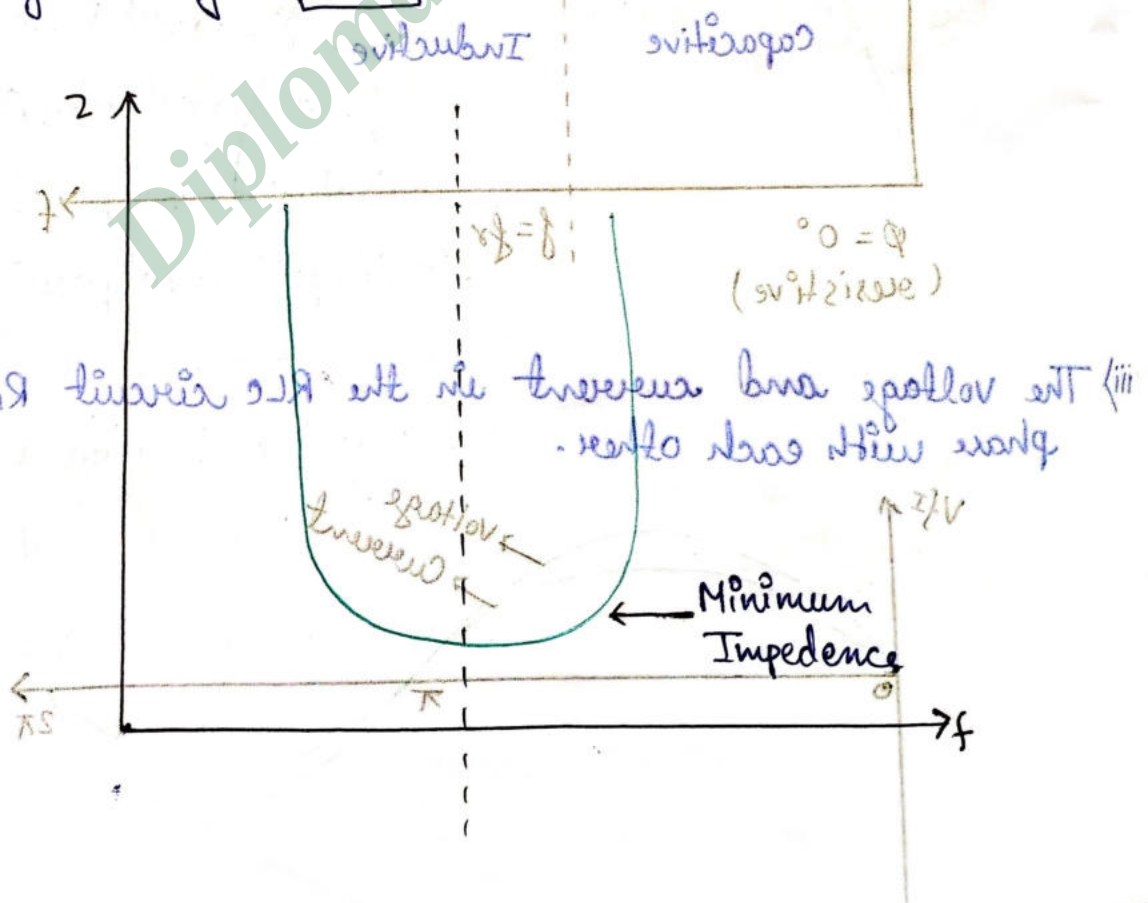v) Impedance of the circuit is minimum and is given by $Z = R$



Expression for Resonant frequency in series RLC circuit.

Inductive reactants = Capacitive reactants

$$X_L = X_C$$

$$\frac{V}{\omega L} = \frac{V}{\omega C}$$

$$\frac{1}{2\pi f L} = \frac{1}{2\pi f C}$$

$$f^2 = \frac{1}{(2\pi)^2 LC}$$

$$f = \frac{1}{\sqrt{(2\pi)^2 LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Resistor = R
Capacitor (Farad) = C
Inductor (Henry) = L
Frequency (Hz) = f
Resonant frequency = f_r
Capacitive reactance = X_C
Inductive reactance = X_L
Current (ampere) = I
Voltage (Volt) = V
Impedance (Z) = Z
Admittance = Y = 1/Z
Conductance = G = 1/R
Susceptance (Inductor) = B
Susceptance (Capacitor) = S
Quality factor = Q
Angular frequency $\omega = 2\pi f$
Power factor = cos ϕ
Power factor angle = ϕ
Impedance = Z
Modulus / Magnitude = | |

Symbols with Names

R = Resistor.

C = Capacitor (Farad)

L = Inductor (Henry).

f = Frequency (Hz)

f_r = Resonant frequency.

X_C = Capacitive Reactance.

X_L = Inductive Reactance.

I = Current (ampere).

V = Voltage (Volt).

Z = Impedance (Ω)

Y = Admittance = $Y = \frac{1}{Z}$

G = Conductance = $G = \frac{1}{R}$.

B_L = Susceptance (Inductor).

B_C = Susceptance (Capacitor).

Q = Quality factor.

ω = Angular frequency $\omega = 2\pi f$

$\cos \phi$ = Power Factor.

$\tan^{-1}()$ = P. Power factor angle.

j = Imaginary.

$||$ = Mode / Magnitude.

P = Total Power

S = Apparent Power

V_R = Voltage across resistor.

V_L = Voltage across Inductor.

V_C = Voltage across Capacitor.

$$\frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$\frac{1}{\omega L} = \frac{1}{2\pi f L}$$

$$\frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$\frac{1}{\omega L} = \frac{1}{2\pi f L}$$