

Unit: 04

Attenuator.....

Date:- 16/01/25

> Attenuator:-

Attenuation is define as loss of power in a transmission line or an electrical network.

Attenuation is expressed as either in Neper (N) or decibel (dB) notation.

Attenuators are either of fixed value or adjustable value types. Generally fixed attenuators provide constant attenuation are called as pads.

In communication various elements are used in the system while transmitting AC power from sending point to receiving point then the system introduce losses of power at various points.

4 Terminal Network

Let input and output power be P_1 and P_2 respectively. The network introduced between generator and load may provide loss or gain in power. Let the ratio of input power to output power i.e. P_1/P_2 be M .

If M is greater than unity then network introduce loss. If M is less than unity then the network introduce gain.

If n number of n/w connected in cascade then overall ratio obtained by multiplying individual power ratio of network. Let M_1 to $M_{(n-1)}$ be individual input power to O/p power for $(n-1)$ network respectively. Then

$$(1) \frac{P_1}{P_n} = \frac{P_1}{P_2} \times \frac{P_2}{P_3} \times \frac{P_3}{P_4} \times \dots \times \frac{P_{(n-1)}}{P_n}$$

$$M = M_1 \times M_2 \times M_3 \times \dots \times M_{(n-1)}$$

This complex calculation to made simple expressed the equation in logarithmic scale. This enables addition of power ratio in the logarithmic scale instead of multiplication. The logarithmic unit employed as 'BELL'.

$$\text{Power ratio in bell} = \log_{10} \left(\frac{P_1}{P_2} \right)$$

BELL unit is too large. Therefore small unit called decibel is introduced.

$$1 \text{ bell} = 10 \text{ decibel}$$

Power ratio expressed in decibel.

$$D = \log_{10} \left(\frac{P_1}{P_2} \right)$$

If $\frac{P_1}{P_2} > 1$ then D will be positive which indicates power loss.

If $\frac{P_1}{P_2} < 1$ the D will be negative which indicates power gain.

→ The power ratio can be expressed as decibel.


$$D = 10 \log_{10} \left(\frac{P_1}{P_2} \right)$$

Anti log $\frac{D}{10} = \log_{10} \left(\frac{P_1}{P_2} \right)$

$$\text{Anti log } \frac{D}{10} = \frac{P_1}{P_2}$$

usually power ratio are expressed in decibel but it is possible to expressed voltage and current ratio in decibel. If the resistive components of generator and load impedance are equal. Similarly neper is usually used to expressed current ratio but it is possible to express power ratio in neper if the resistive component of generator and load impedance are equal.

→ Suppose a four terminal network:-

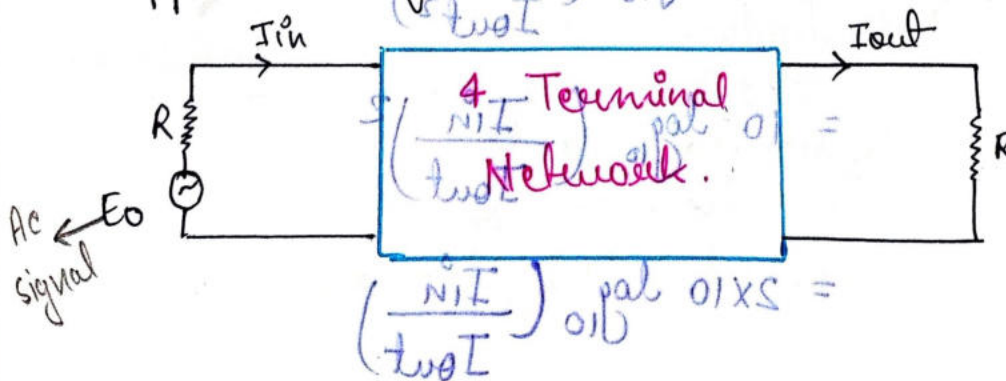

Day:- Friday Date: 17/10/21

→ If Power entering a P_{in} and that leaving a network is P_{out} then the attenuation in decibel is defined as

$$\text{Attenuation (dB)} = 10 \log_{10} \left(\frac{P_{in}}{P_{out}} \right)$$

→ If the current entering a network is I_{in} and that leaving the network is I_{out} . Then the attenuation in Neper is defined as.

$$\text{Attenuation (Neper)} = \ln \left(\frac{I_{in}}{I_{out}} \right)$$

→ Condition of equal resistance we can write

$$\text{Attenuation} = 10 \log_{10} \left(\frac{P_{in}}{P_{out}} \right)$$

$$= 10 \log_{10} \left(\frac{I_{in}^2 R}{I_{out}^2 R} \right)$$

$$= 10 \log_{10} \left(\frac{I_{in}^2}{I_{out}^2} \right)$$

$$= 10 \log_{10} \left(\frac{I_{in}}{I_{out}} \right)^2$$

$$= 2 \times 10 \log_{10} \left(\frac{I_{in}}{I_{out}} \right)$$

$$(11) \text{ neper} = 20 \log_{10} \left(\frac{I_{in}}{I_{out}} \right)$$

$$\text{Attenuation} = 20 \log_{10} \left(\frac{E_{in}}{E_{out}} \right)$$

$$\text{Attenuation (Neper)} = \ln \left(\frac{I_{in}}{I_{out}} \right)$$

$$= \ln \left(\frac{E_{in}}{E_{out}} \right)$$

$$= \frac{1}{2} \ln \left(\frac{P_{in}}{P_{out}} \right)$$

Definition of Neper and Decibel:-

i) Neper (N):- The Neper (N) is similar to the decibel (dB). It is unitless and is used to express ratios. The Neper uses the natural logarithm and invented by 'John Napier'.

$$dB = 20 \log (a/b)$$

$$N = \ln (a/b)$$

$$\frac{dB}{N} = \frac{20 \log (a/b)}{\ln (a/b)}$$

$$= \frac{20}{\ln(10)} = 8.685$$

$$\text{Note} = \ln(x) = \log(x) \times \ln(10).$$

* Attenuation (dB) = $8.685 \times$ attenuation (N).


* Attenuation (N) = $0.1151 \times$ attenuation (dB).

ii) Decibel (DB) :- The decibel is a logarithmic unit of measurement that expresses the magnitude of a physical quantity relative to a specified or implied reference level.

» Classification of Attenuator :-

Attenuator are basically classified as fixed and variable attenuator. Fixed attenuator are some times called Pads. These pads are symmetrical or asymmetrical network.

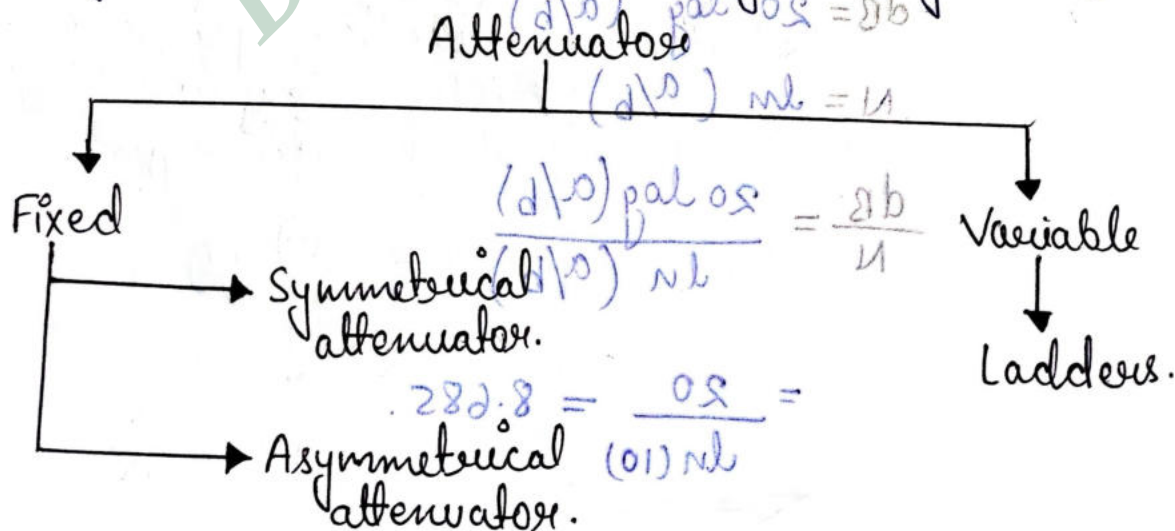- The symmetrical attenuator are either T, π lattice or bridged-T network.
- Asymmetrical network are generally L-network.



→ Variable attenuators are ladder types and continuously variable type network.

An example of a ladder type attenuator is a signal generator where input and output voltage or current ratio are to be reduced in known ratio.

Let in a network the resistance is R_1 and the total resistance is R_2 . The ratio of the output voltage to the input voltage is $\frac{V_2}{V_1}$.



$$V = \alpha + \beta$$

$$\frac{R_1}{5} \leftarrow \frac{5}{5}$$


Date:- 27/01/25Day:- Monday

» Symmetrical T-Attenuator

In attenuator whose shape looks like the english alphabet "T" is called T-type attenuator.

→ In this attenuator the resistance in the series are equal and also the total input resistance (R_{in}) and output resistance (R_o) are also equal.

* Circuit Diagram:-

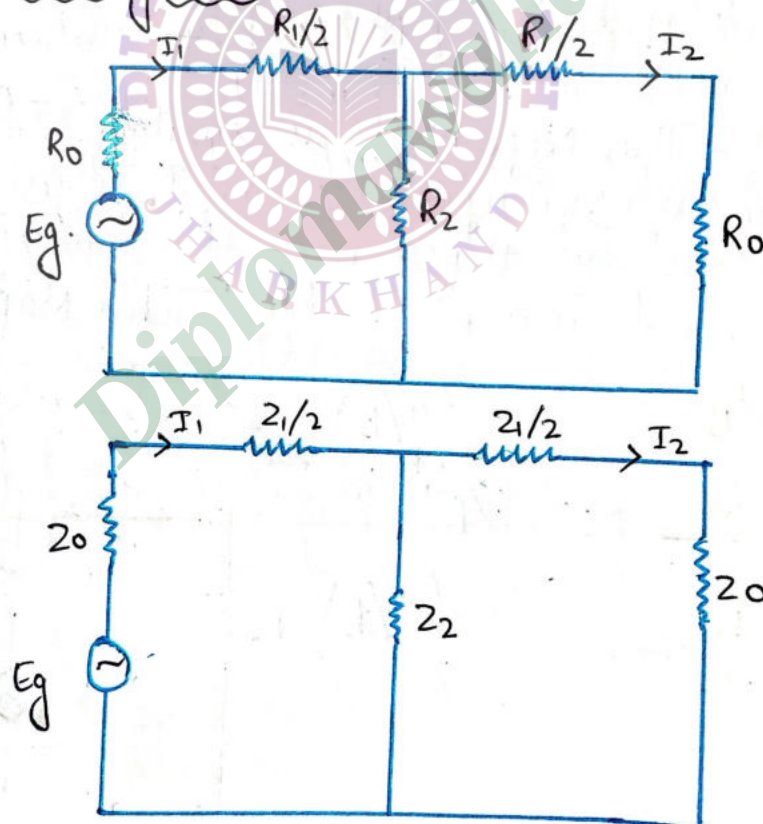

$$Z_o \rightarrow R_o$$

$$\frac{Z_1}{2} \rightarrow \frac{R_1}{2}$$

$$Z_2 \rightarrow R_2$$

$$\gamma = \alpha + j\beta$$

$$\gamma = \alpha$$

$$N = \frac{I_1}{I_2}$$

$$\frac{0.85}{\frac{1}{N} - 1} =$$

R_0 = Characteristics Resistance. $\frac{0.85}{\frac{1}{N} - 1}$ design Impedence.

$$R_1 = (R_0, N)$$

$$R_2 = (R_0, N)$$

$$\left(\frac{1.15}{1 - 0.85} \right) 0.85 = 5.9$$

→ In symmetrical T-Network, (formulas,)

$$\frac{Z_1}{2} = Z_0 \tanh \frac{\gamma}{2}$$

$$\frac{Z_2}{2} = \frac{Z_0}{\sinh \gamma}$$

$$\frac{R_1}{2} = R_0 \tanh \frac{\alpha}{2}$$

$$R_2 = \frac{R_0}{\sinh \alpha}$$

Note:-

$$e^\alpha = N = \frac{I_1}{I_2}$$

$$R_1 = R_0 \left[\frac{e^{\alpha/2} - e^{-\alpha/2}}{e^{\alpha/2} + e^{-\alpha/2}} \right]$$

$$= R_0 \left[\frac{e^{\alpha/2} - e^{-\alpha/2}}{e^{\alpha/2} + e^{-\alpha/2}} \right]$$

$$= R_0 \left[\frac{e^\alpha - 1}{e^\alpha + 1} \right]$$

$$\frac{R_1}{2} = R_0 \left[\frac{N - 1}{N + 1} \right] \quad \text{--- (1)}$$

$$\begin{aligned} * R_2 &= \frac{R_0}{\sinh \alpha} = \frac{R_0}{\left(\frac{e^\alpha - e^{-\alpha}}{2} \right)} \\ &= \frac{R_0}{\frac{e^\alpha - e^{-\alpha}}{2}} = \frac{2 R_0}{e^\alpha - e^{-\alpha}} \end{aligned}$$

$$= \frac{2R_0}{N - \frac{1}{N}}$$

$$\frac{I_1}{I_2} = N$$

$$= \frac{2R_0}{\frac{N^2 - 1}{N}} \quad \text{Characteristic Resistance } R_0 = 50 \Omega$$

$$R_2 = R_0 \left(\frac{2N}{N^2 - 1} \right) \quad \text{--- (II)}$$

$$(11, 0.8) = 1.8$$


$$(11, 0.8) = 5.8$$

→ Eqn (I) and (II) are design eqn in symmetrical T-attenuator.


» Symmetrical π -attenuator :-

An attenuator whose shape look like π is called π -type attenuator. In this attenuator resistance in the shunt are equal and also the input resistance is equal to the output resistance.

* Circuit Diagram :-

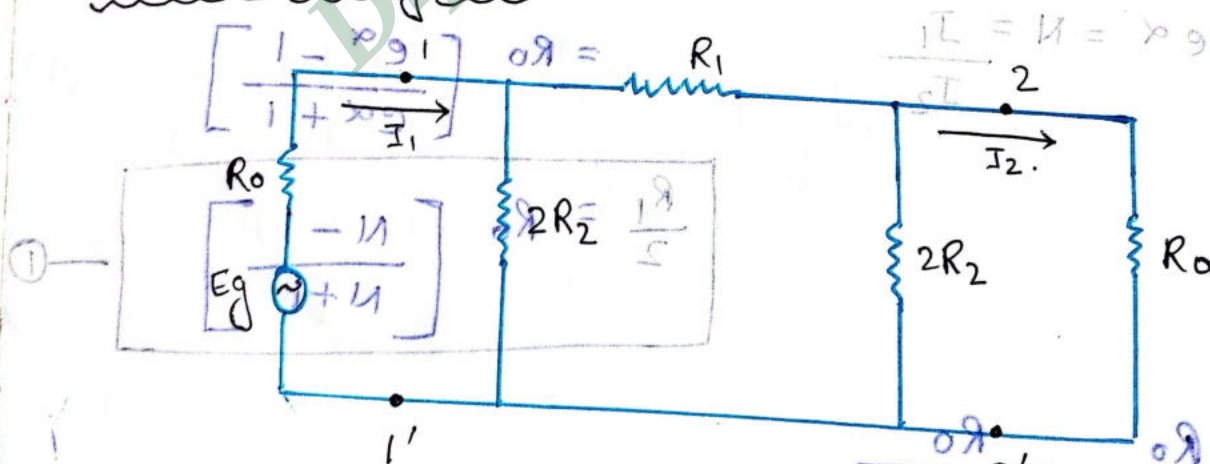
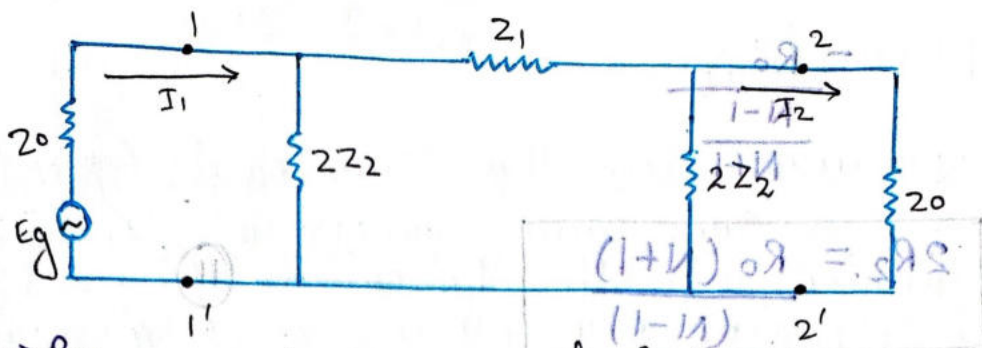
$$\frac{R_0}{\frac{N^2 - 1}{N}} = \frac{R_0}{\frac{N^2 - 1}{N}} = \frac{R_0}{\frac{N^2 - 1}{N}}$$



$$Z_0 \rightarrow R_0$$

$$R_1 \rightarrow Z_1$$

$$2R_2 \rightarrow 2Z_2$$

$$Y = \alpha + j\beta$$

$$Y = \alpha$$

→ In symmetrical π -Networks —

$$Z_1 = Z_0 \sinh Y$$

$$2Z_2 = \frac{Z_0}{\tanh Y/2}$$

$$R_1 = R_0 \sinh \alpha$$

$$2R_2 = \frac{R_0}{\tanh \alpha/2}$$

$$\rightarrow R_1 = R_0 \left[\frac{e^\alpha - e^{-\alpha}}{2} \right]$$

$$= R_0 \left[\frac{N - \frac{1}{N}}{2} \right]$$

$$= R_0 \left[\frac{\frac{N^2 - 1}{N}}{2} \right]$$

$$R_1 = R_0 \left[\frac{N^2 - 1}{2N} \right] \quad \text{————— (1)}$$

$$\rightarrow 2R_2 = \frac{R_0}{\tanh \frac{\alpha}{2}}$$

$$= \frac{R_0}{\frac{e^{\alpha/2} - e^{-\alpha/2}}{e^{\alpha/2} + e^{-\alpha/2}}}$$

$$= \frac{R_0}{\frac{e^\alpha - 1}{e^\alpha + 1}}$$

$$= \frac{R_0}{\frac{N-1}{N+1}}$$

$$2R_2 = \frac{R_0(N+1)}{(N-1)} \quad \text{--- (11)}$$

→ Eqn ① and ⑪ are design eqn in symmetrical π -Network.

$$R_0 \sin \alpha = 1$$

$$\frac{R_0}{\sin \alpha} = 1$$

$$R_0 = \frac{e^{\alpha} - e^{-\alpha}}{2}$$

$$R_0 = \left[\frac{1 - \frac{1}{N}}{2} \right]$$

$$R_0 = \left[\frac{1 - \frac{1}{N}}{\frac{N}{2}} \right]$$

$$R_0 = \left[\frac{1 - \frac{1}{N}}{2N} \right]$$

$$R_0 = \frac{e^{\alpha} - e^{-\alpha}}{2}$$

$$R_0 = \frac{e^{\alpha} - e^{-\alpha}}{2}$$