

1056**Code : 9EC-31**Register
Number

--	--	--	--	--	--	--

III Semester Diploma Examination, Nov./Dec. 2014**ANALOG ELECTRONIC CIRCUITS****Time : 3 Hours]****[Max. Marks : 100**

Note : (i) Question No. – 1 is *compulsory*.
 (ii) Answer any **two** full questions each from remaining sections.

1. (a) Fill in the blanks : 5

- (i) IC 723 is an example of _____ voltage regulator.
- (ii) Maximum Efficiency of Series fed Class-A amplifier is _____.
- (iii) CMRR stands for _____.
- (iv) The Electronic circuit which produces a periodic waveform is called _____.
- (v) The basic instrumentation amplifier has _____ no. of amplifiers.

(b) Write a note on Schmitt trigger circuit. 5

SECTION – A

2. (a) Explain with neat diagram the operation of SMPS. 8

(b) Explain the operation of the half-wave rectifier. 7

3. (a) In a half-wave rectifier circuit, the secondary voltage of transformer is 6 volts. Find the dc voltage V_{dc} and ripple factor of circuit. 6

(b) Explain off-line UPS System with diagram. 5

(c) List different types of feedback principles. 4

4. (a) State & Explain Barkhausen criterion for sustained oscillations. 6

(b) Explain the operation of Colpitts Oscillator with neat circuit diagram. 6

(c) What is piezoelectricity ? 3

[Turn over

SECTION – B

5. (a) What is biasing ? Explain voltage divider biasing for FET. 7
 (b) What is operating point ? Explain it. 5
 (c) List the types of power amplifier. 3

6. (a) Explain the operation of Complementary push-pull class-B amplifier with diagram. 7
 (b) Explain the operation of class-C amplifier. 5
 (c) List the disadvantages of class-B amplifier. 3

7. (a) Explain the operation of Simple Shunt-Clipper with neat circuit and waveforms. 6
 (b) Explain the operation of R-C integrator circuit with waveforms. 5
 (c) List the applications of clippers and damps. 4

SECTION – C

8. (a) Derive an expression for voltage gain of inverting amplifier using Op-Amp. 6
 (b) Draw and explain block diagram of Op-Amp. 5
 (c) List the characteristic of ideal- Op-Amp. 4

9. (a) Explain the operation of differentiator using Op-Amp. 6
 (b) The Summing amplifier using Op-Amp has the following inputs :
 5V, 3V and 1V and feedback resistor R_F is 20 k Ω and each input resistor is 2 k Ω . Calculate the o/p voltage. 5
 (c) Define the following terms with respect to Op-Amp :
 (i) Input offset voltage
 (ii) Slew rate
 (iii) Input bias current
 (iv) Gain-bandwidth product 4

10. (a) Describe the Instrumentation amplifier circuit. 7
 (b) Explain the operation of PLL with diagram. 4
 (c) List the applications of PLL. 4
