



Analog Electronics

DIPLOMA WALLAH


EE/EEE

Jharkhand University Of Technology (JUT)


Unit 05

A. Opto-Electronic Devices & Opto-Couplers

A1. Light-Emitting Diode (LED) & IR LED

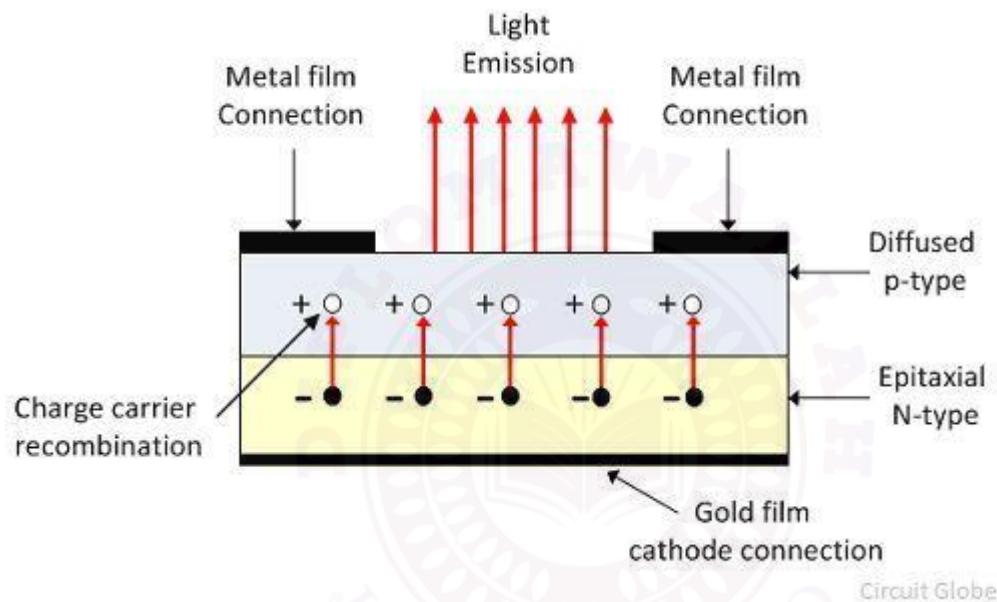


Circuit Globe

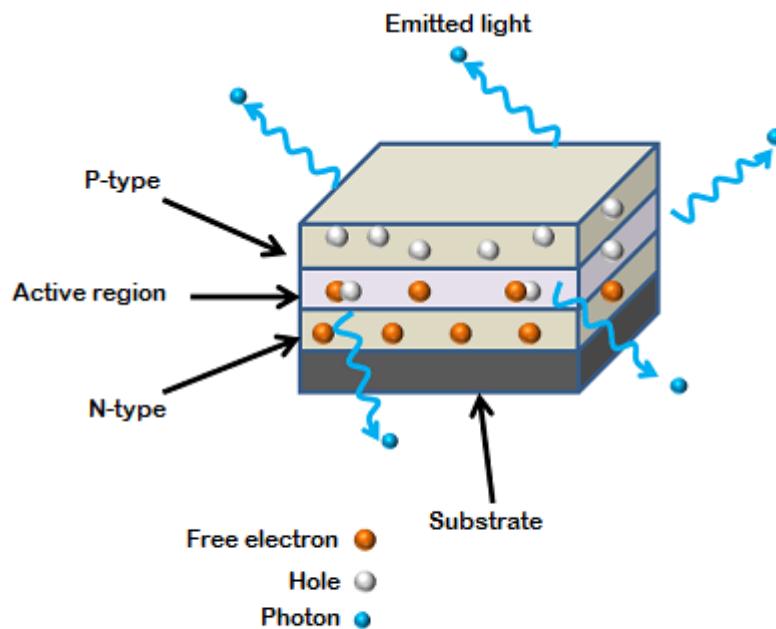

Construction of LED


WORKING PRINCIPLE OF LED

BYJU'S
The Learning App

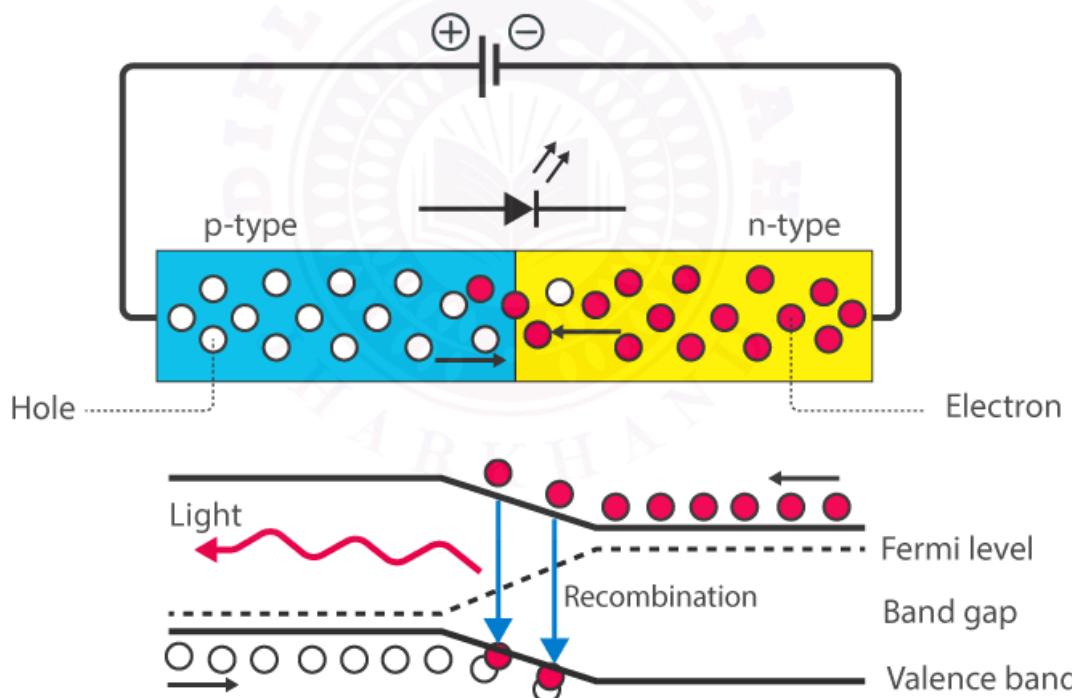


© Byjus.com

LED Working Principle

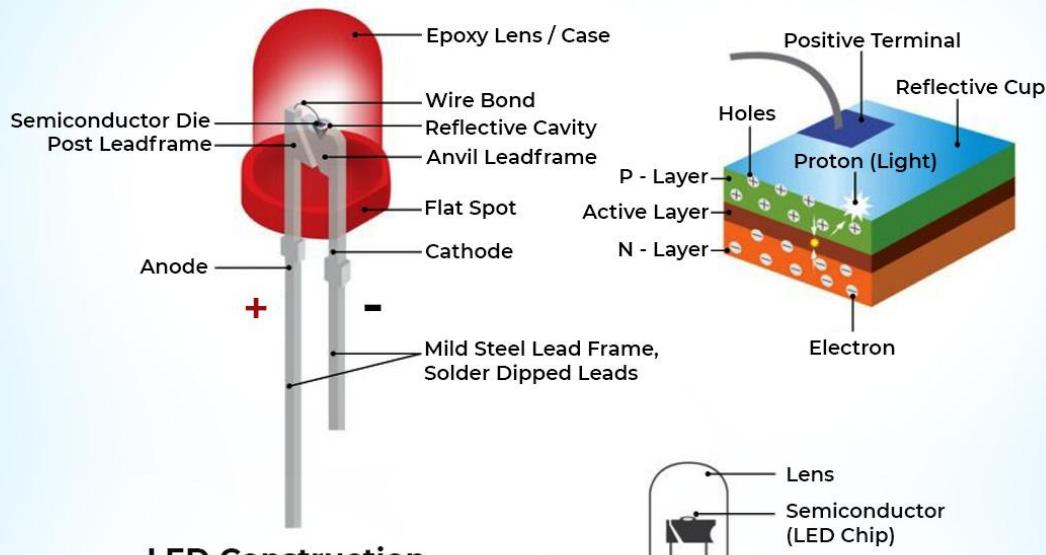

LED Construction

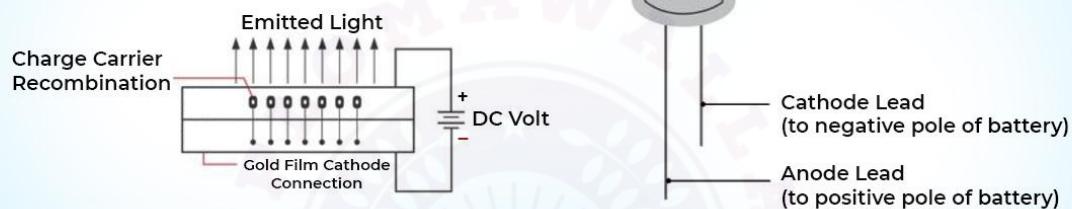


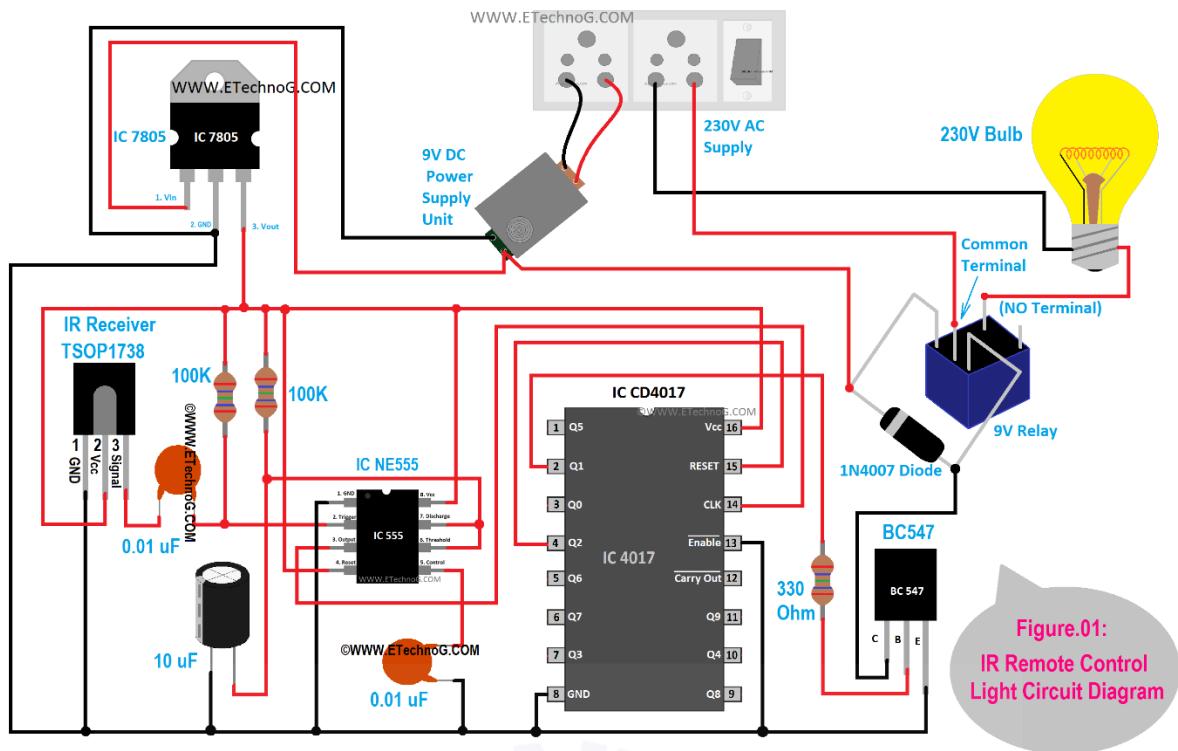


Figure.01:
IR Remote Control
Light Circuit Diagram

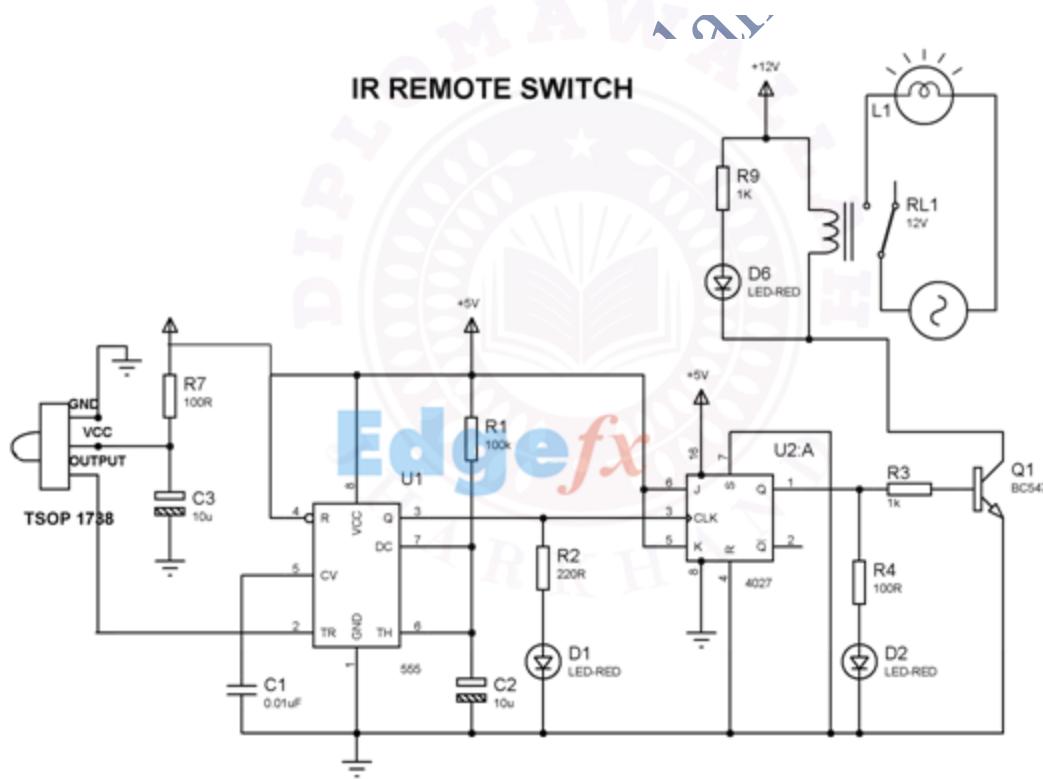

Construction & Materials

- An LED is basically a p-n junction diode made of compound semiconductor materials such as GaAs (gallium arsenide), GaP (gallium phosphide), AlGaInP etc. ([Electrical 4U](#))



- The LED die (junction) is encapsulated in epoxy resin (which often acts as a lens) and the leads are anode (+) and cathode (-).
- IR LED is similar construction but emits in the infrared spectrum rather than visible light – used in remote controls, IR communication, sensing.

Working Principle

- The working is based on *electroluminescence*. When the LED is forward-biased (anode positive with respect to cathode) electrons from the n-region and holes from the p-region recombine in the depletion/active region. When they recombine, energy is released as photons (light) rather than just heat. ([Electrical 4U](#))
- The wavelength (colour) of light depends on the band-gap of the semiconductor material used: the larger the band-gap, the shorter the wavelength (towards blue/UV). ([Wikipedia](#))
- For an IR LED, the emission is invisible to human eye but used for sensors, remote controls etc.

Characteristics

- Forward voltage (V_F): the voltage required to forward-bias the LED. E.g., red $\sim 1.8\text{--}2.2\text{ V}$, blue/white $\sim 3\text{--}3.6\text{ V}$.
- Forward current (I_F): maximum continuous current (often $\sim 10\text{--}30\text{ mA}$ for indicator LEDs, higher for high-power LEDs). Must not exceed, else damage. ([Basic Electronics Tutorials](#))
- Efficiency: Ratio of light output to electrical input energy (LEDs are much more efficient than incandescent bulbs because less heat wasted). ([The Department of Energy's Energy.gov](#))
- Lifetime: Solid-state device, durable, shock resistant.
- Polarity matters: Anode/cathode must be correct – an LED only emits light when correctly forward-biased.

Applications

- Indicator lights, displays (seven-segment, dot-matrix), back-lighting.
- IR LED: remote controls, IR remote sensors, optical communication.


- Lighting: high-power LEDs for lighting, automotive headlamps.
- Fibre-optics, signalling, visual displays.


Design Tips

- Always use a **series resistor** to limit current:


$$R = \frac{V_{\text{supply}} - V_F}{I_F}$$
- where (V_F) is forward voltage, (I_F) desired current. ([Basic Electronics Tutorials](#))
- Check that the LED's power dissipation and thermal management are adequate (especially high-power types).
- Match emission wavelength (for IR LED) to the detector's sensitivity (photodiode/phototransistor) when designing sensors.


A2. Photodiode & Phototransistor

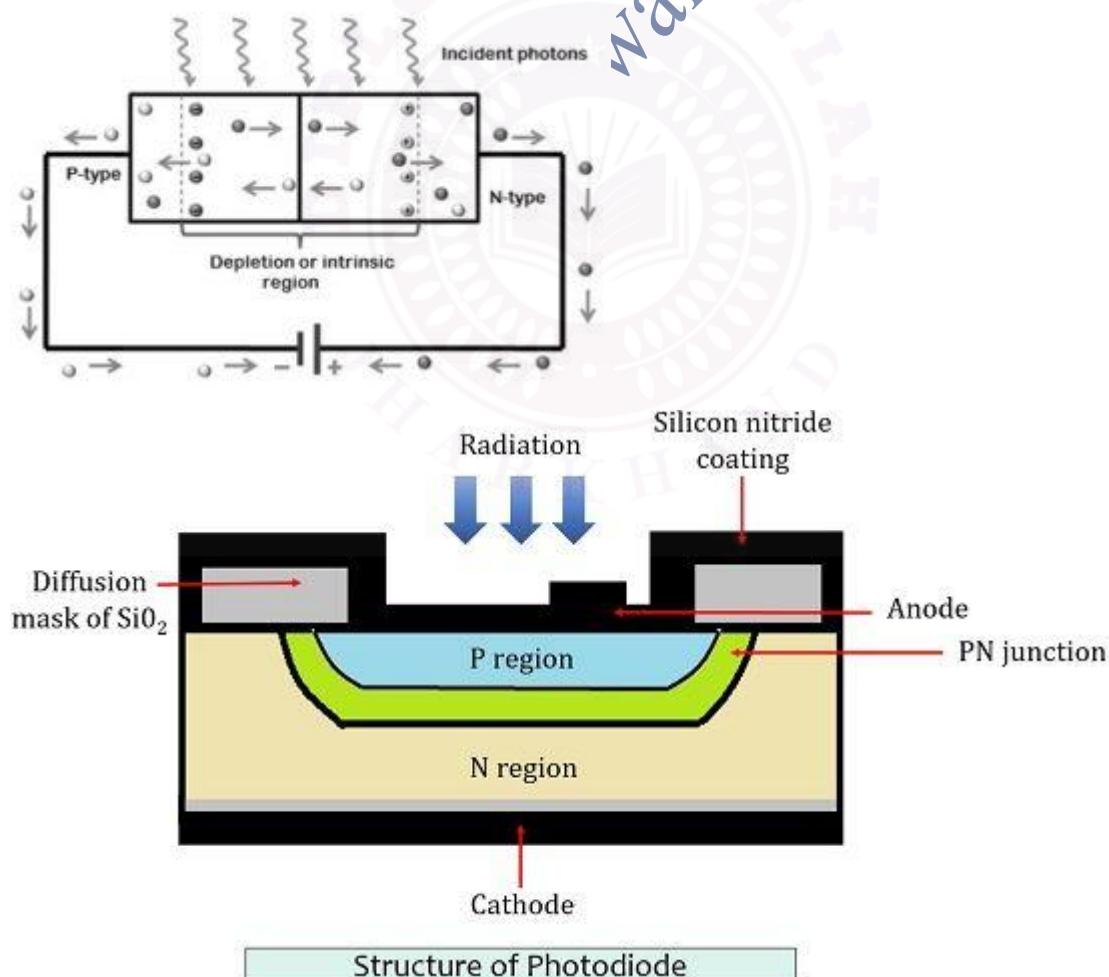

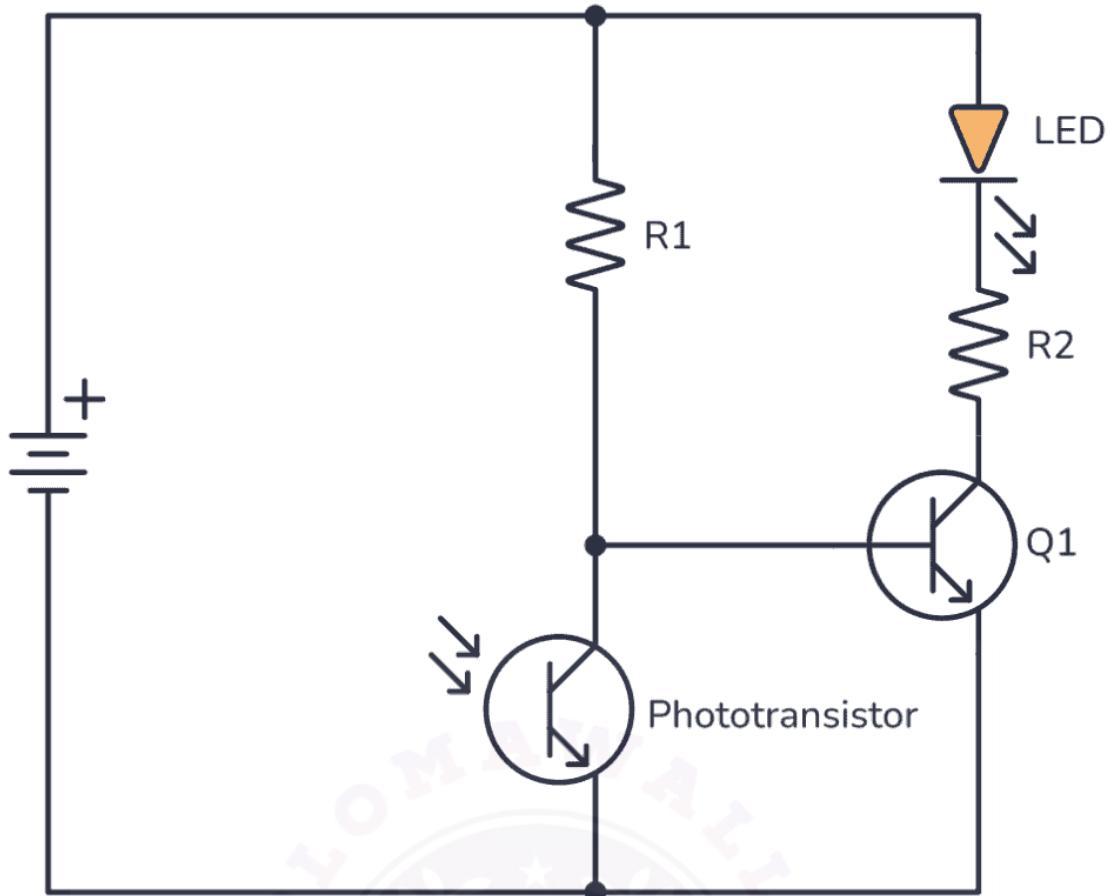

**Phototransistor
Symbol**

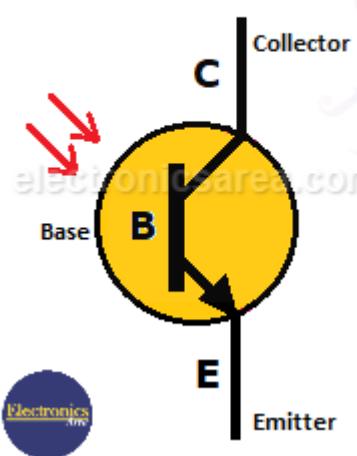

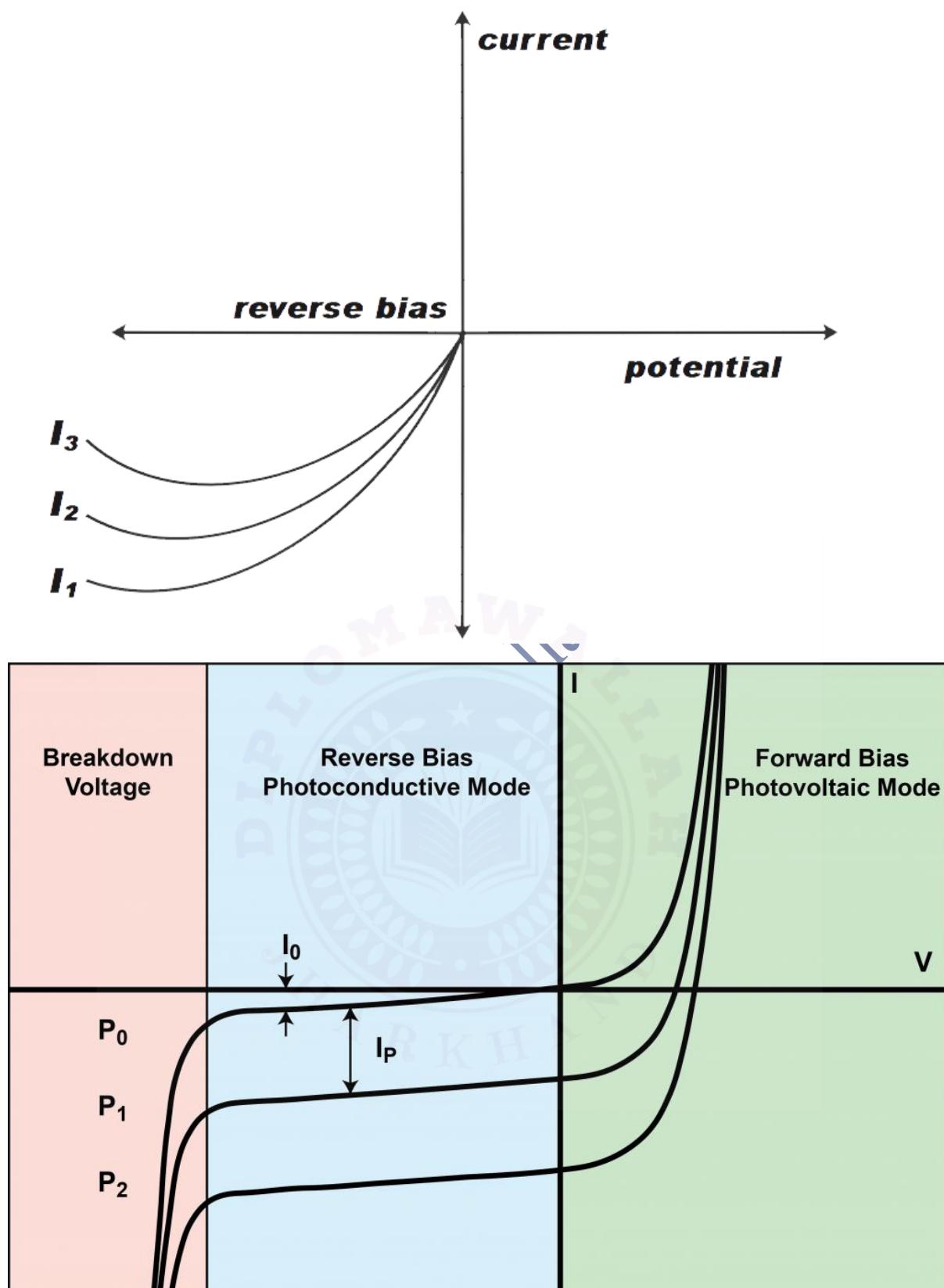

Photodiode

- A photodiode is a p-n or p-i-n semiconductor device whose junction is exposed (or behind a transparent window) so that



incident light generates electron-hole pairs in the depletion region. ([Homemade Circuits](#))

- Works commonly in *reverse bias* (photoconductive mode): light increases current under reverse bias; the photocurrent is proportional to incident light intensity.
- Characteristics: responsivity (A/W), dark current (current in absence of light), response time (how fast it responds).
- Applications: light sensors, optical communication receivers, solar cells (large area variant), ambient light sensing.



Phototransistor

- A phototransistor is essentially a transistor whose base is driven by light (rather than by an external base current). The light-induced base current is amplified by transistor action, so the device gives higher gain compared to photodiode. ([ORIENT COMPONENTS](#))
- It is slower in response than photodiode (because of transistor's stored charge), but simpler to interface and gives higher output current.
- Applications: IR remote receivers, light-barrier sensors, opto-coupler internal detectors.


Comparison

Device	Speed	Gain	Output current	Typical use
Photodiode	Very fast	Low (≈ 1)	Smaller	High-speed detection
Phototransistor	Moderate	High (transistor gain)	Higher	General light sensing


A3. Opto-Couplers (Opto-Isolators)

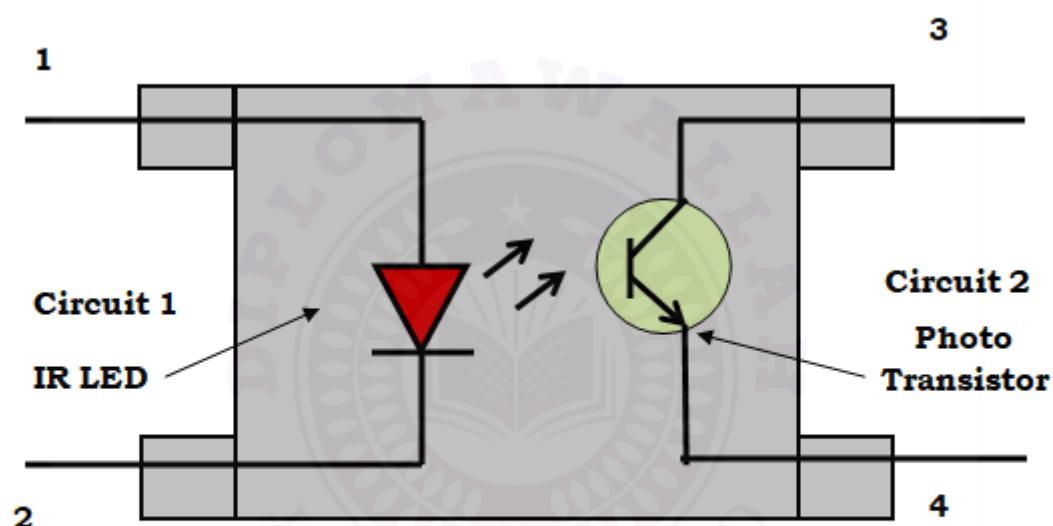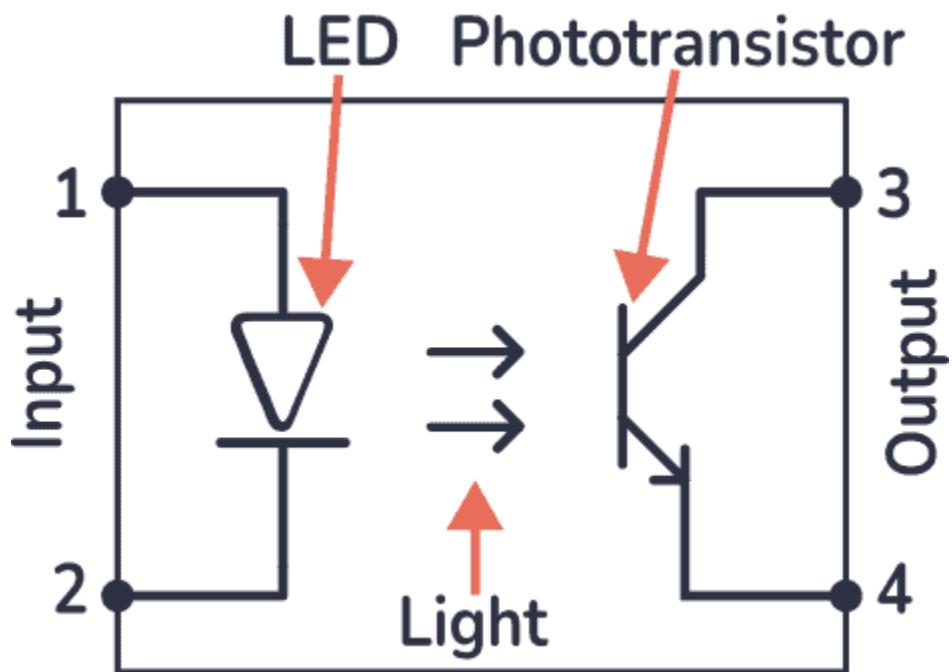


Learn Electronics with me

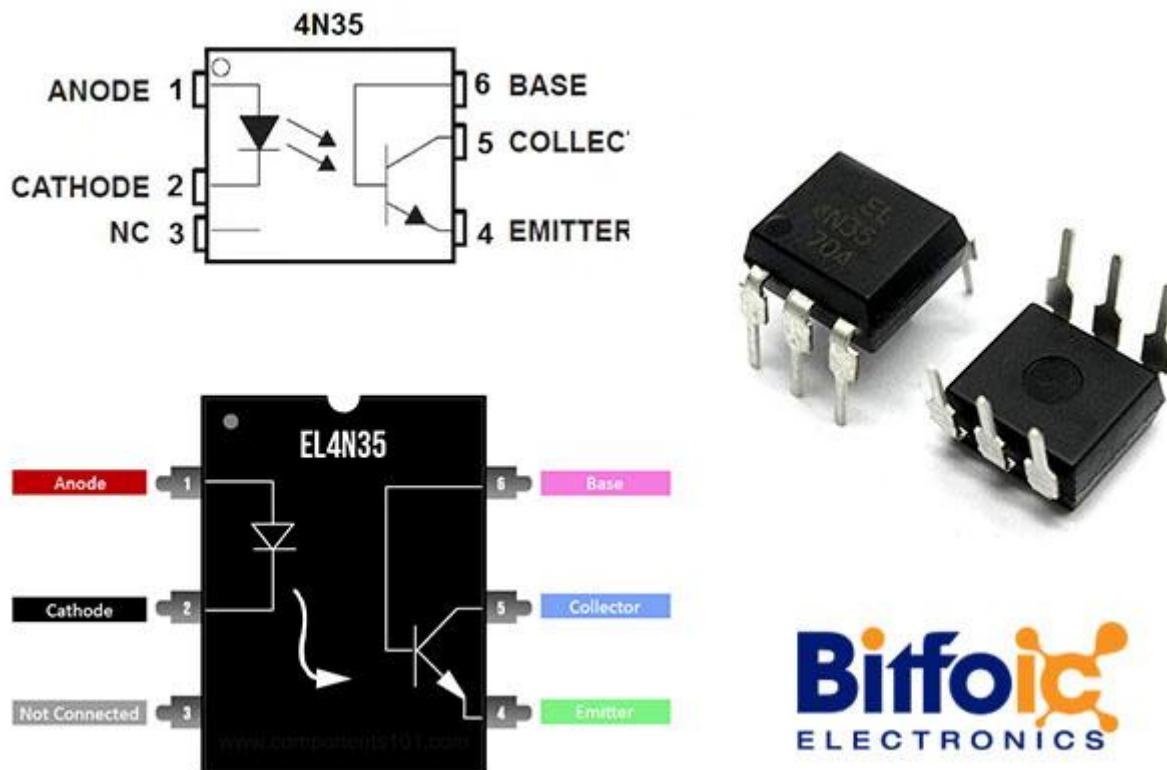

4N35 Optocoupler IC

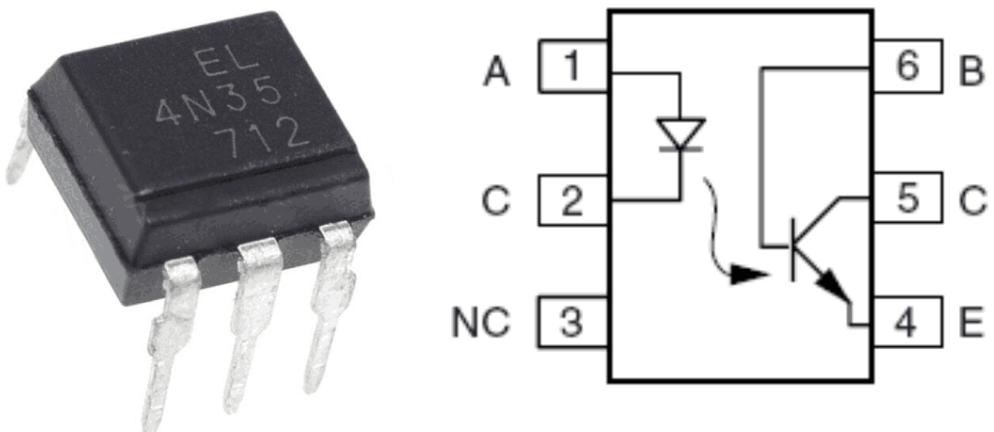

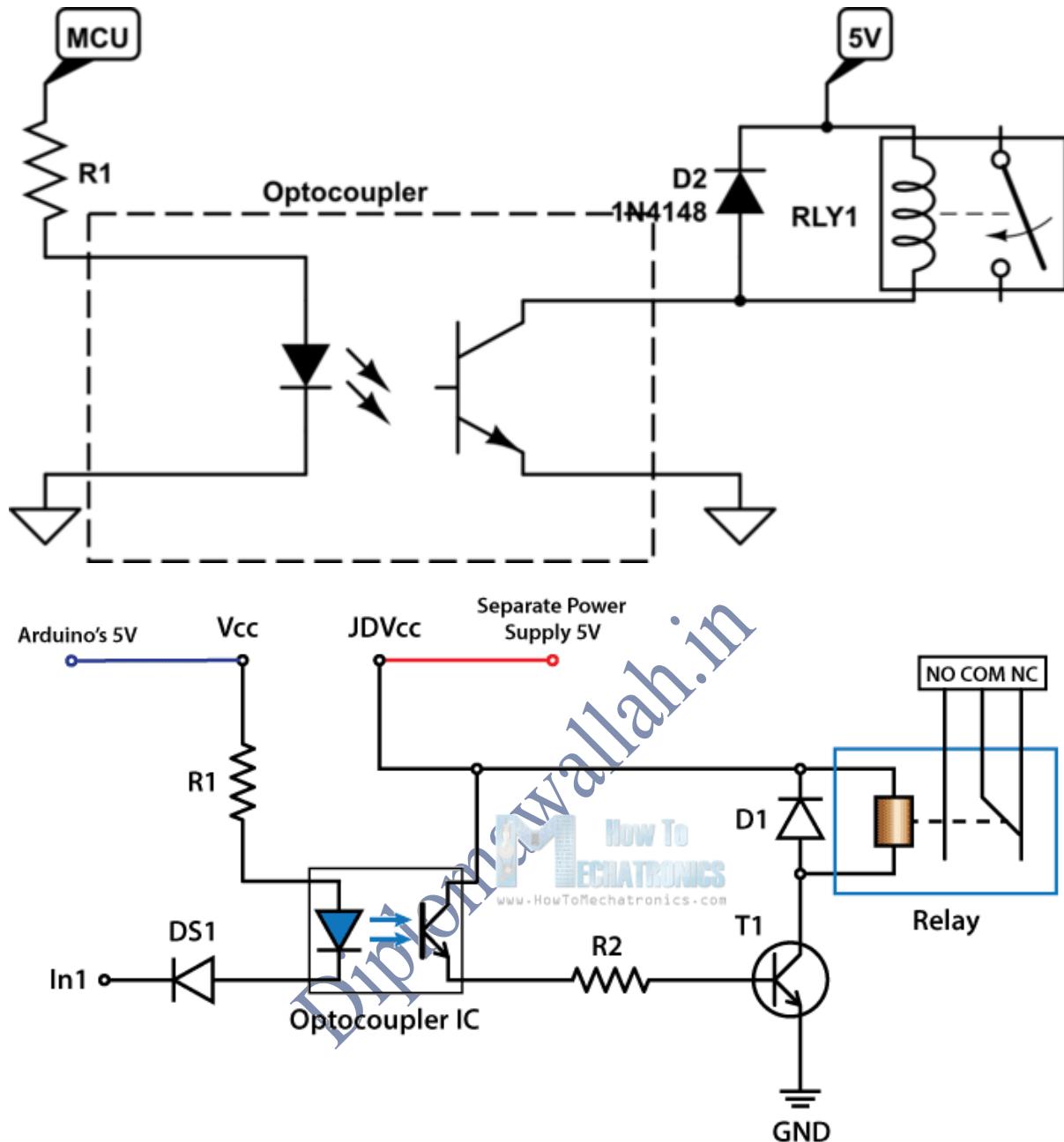

Definition & Function

- An opto-coupler (also called opto-isolator) is a component that transfers electrical signals between two **electrically isolated** circuits using light as the coupling medium. It typically has an LED on the input side and a photodiode or phototransistor (or photo-SCR/triac) on the output side, all enclosed in a single package. ([Basic Electronics Tutorials](#))
- Because there is no direct electrical connection, opto-couplers provide galvanic isolation; important in protecting low-voltage logic from high-voltage mains, noise, ground loops.

Working

- When the LED is driven by input signal, it emits light. That light falls on the detector (phototransistor or photodiode) causing current to flow in the output circuit.
- As the light is blocked/absent, output side stops conducting; thus the signal is transferred while the two sides remain isolated. ([Inst Tools](#))
- Key parameter: CTR (Current Transfer Ratio) = output detector current / input LED current (typically expressed as a percentage). Also, turn-on/turn-off times, isolation voltage, input/output voltage limits.


Applications

- Isolating microcontroller or digital logic from high-voltage switch circuits or noisy power electronics.
- Telecommunication interfaces, PLCs, power supply feedback, motor drive feedback circuits.
- Isolated signal transfer in medical electronics (safety-critical), industrial instrumentation.


Design Considerations



- Ensure LED drive current is sufficient to get required detector current (based on CTR).
- Check maximum isolation voltage rating.
- Check whether detector is photodiode, phototransistor or triac type depending on AC/DC, speed, and current requirements.
- For faster response, choose LED + photodiode type instead of phototransistor.


A4. Laser Diodes

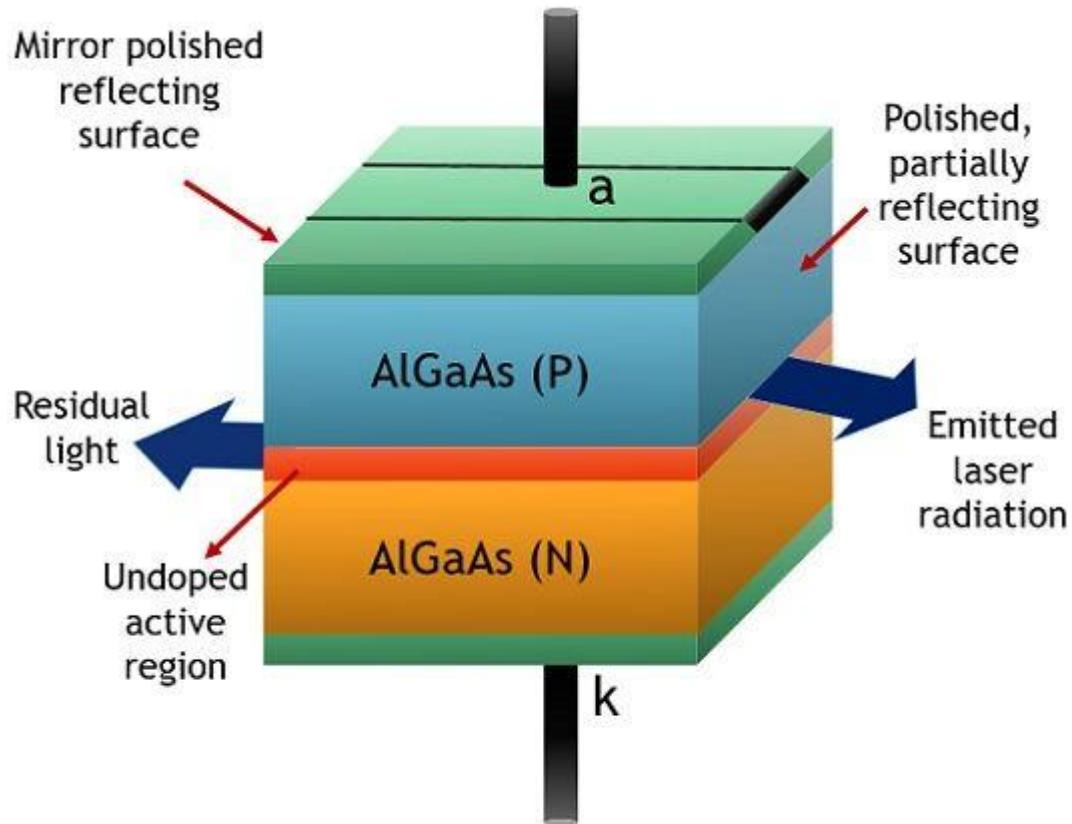

Constructional detail of laser diode

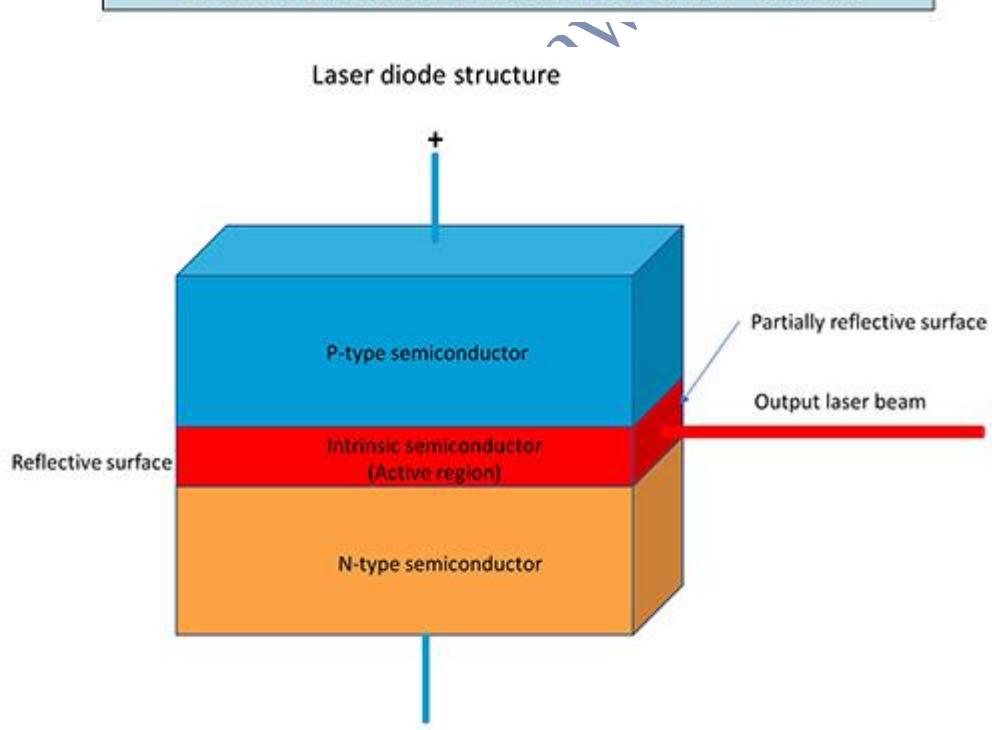

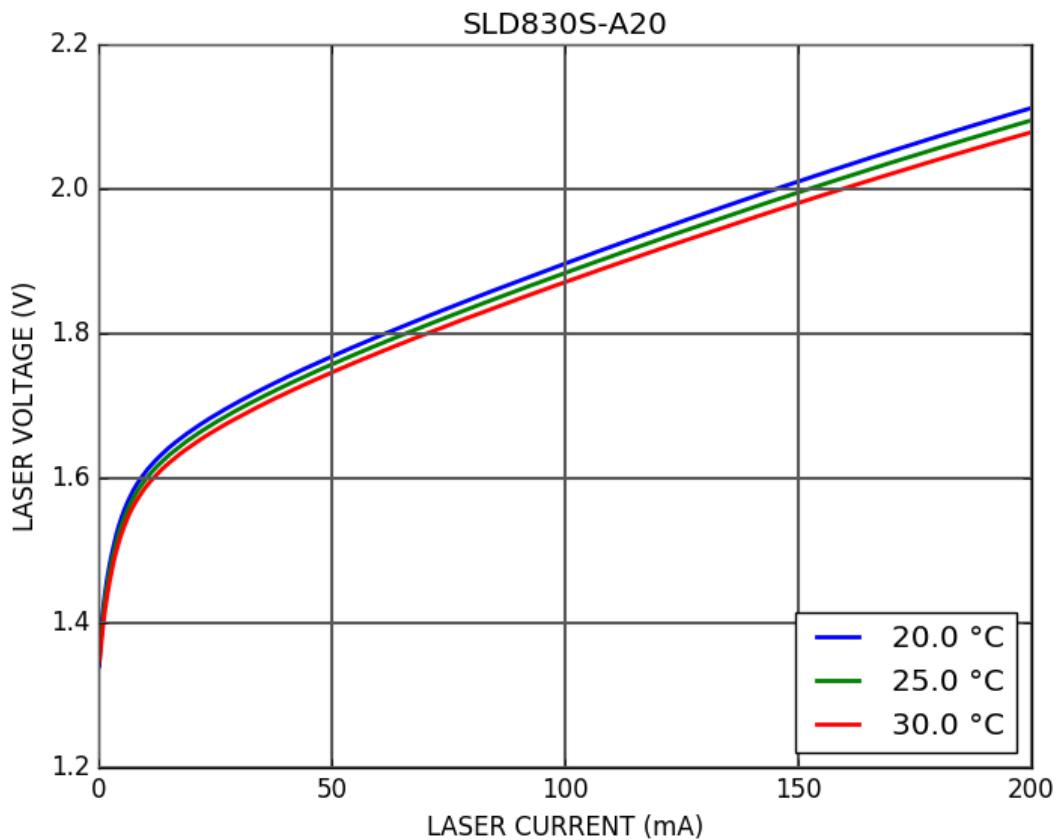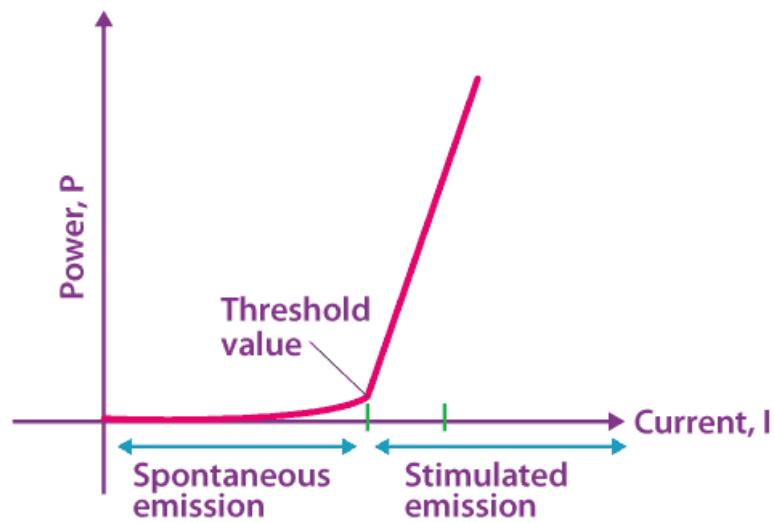

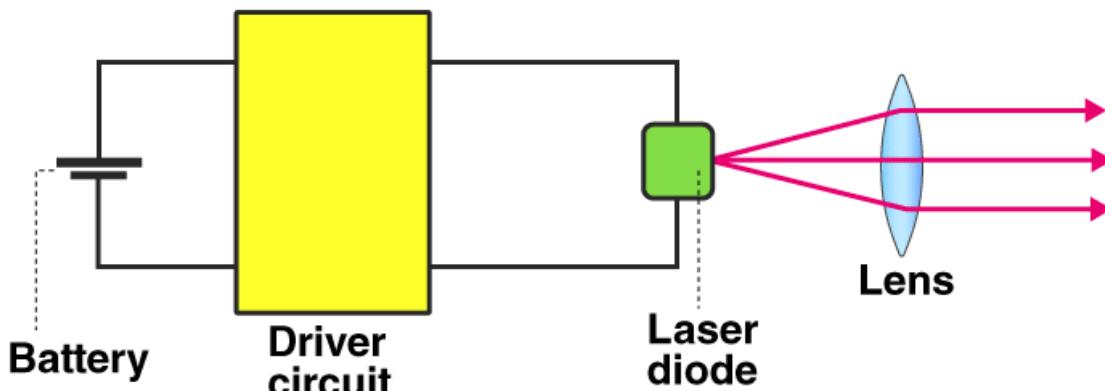

© Byjus.com

Construction & Principle

- A laser diode is a semiconductor diode designed so that the p-n junction (or p-i-n) region acts as a resonant optical cavity; the ends of the chip act like mirrors, enabling stimulated emission of photons that are coherent (same phase), monochromatic and directional.
- When the driving current exceeds a threshold (I_{th}), stimulated emission dominates and lasing occurs. Below that current it behaves like an LED (spontaneous emission).

Characteristics

- Threshold current (I_{th}): minimum current for lasing.
- Slope efficiency: incremental optical power per incremental current above threshold.
- Output wavelength: determined by material and cavity design.
- Narrow beam divergence, coherent output.
- Sensitive to heat: thermal management is critical.

Applications

- Fibre-optics communication, barcode scanners, CD/DVD/Blu-ray players, laser pointers, laser printers, medical surgery lasers, industrial cutting/welding (in higher power diode variants).

- Because laser diodes can modulate at very high frequencies, they're used in high-speed optical links.

Design Tips

- Drive with constant current source (not just constant voltage) because output varies strongly with current and temperature.
- Use proper heat-sink and temperature control (as wavelength and output drift with temperature).
- Use safety precautions (especially with higher power diodes) – laser radiation can damage eyes.

B. Amplifier Topics

B1. Faithful Amplification

- Faithful amplification means the amplifier should reproduce the input signal at its output with **greater amplitude**, but **without distortion**, preserving the waveform shape, frequency, phase (if required).
- To achieve this, the active device (transistor/MOSFET) must be biased so that the input signal amplitude swings around the Q-point without driving the device into cut-off or saturation.
- The bandwidth, linearity, distortion, noise all affect whether amplification is “faithful”.
- In exam context, you should emphasise: stable bias, proper load, minimal clipping, minimal distortion, adequate bandwidth.

B2. Classification of Amplifiers

Based on configuration

- Common-emitter (CE), common-base (CB), common-collector (CC) for BJTs. Each has different input/output impedance, phase shift, gain.
- Multi-stage vs single-stage amplifiers.

Based on power/output stage class

- Class A: Conduction angle 360° (device conducts full cycle). Excellent linearity but poor efficiency ($\approx 20\text{-}30\%$).

- Class B: Conduction $\sim 180^\circ$ each device (two devices typically in push-pull). Higher efficiency ($\sim 78.5\%$ theoretical) but risk of crossover distortion. ([Testbook](#))
- Class AB: Conduction between 180° and 360° ; compromise between linearity and efficiency.
- Class C: Conduction $< 180^\circ$, used primarily in RF where waveform distortion is acceptable.

Based on frequency


- Audio amplifiers (20 Hz – 20 kHz), video amplifiers (MHz), RF amplifiers (MHz-GHz).



Based on duty / signal

- Small-signal amplifiers vs power amplifiers (which drive loads such as loudspeakers, motors etc).


B3. Transistor Common-Emitter (CE) Amplifier & Push-Pull Amplifier

CE Amplifier – Structure & Working

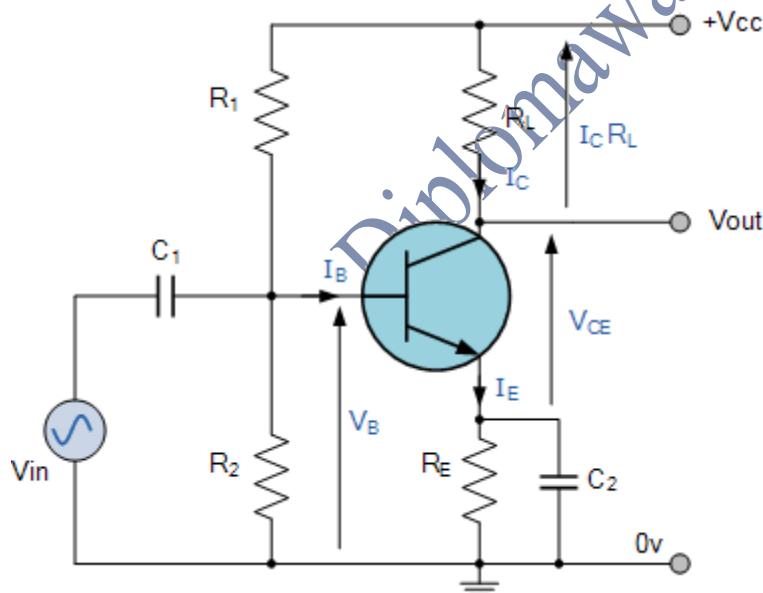

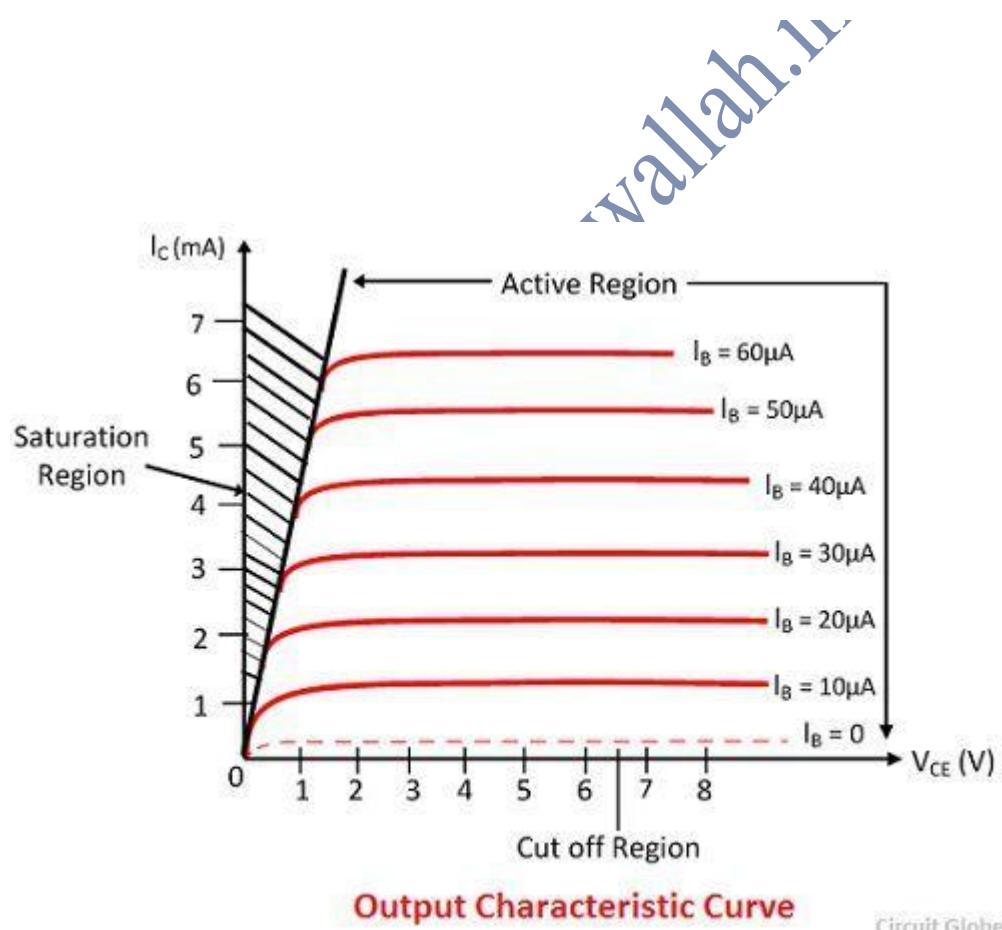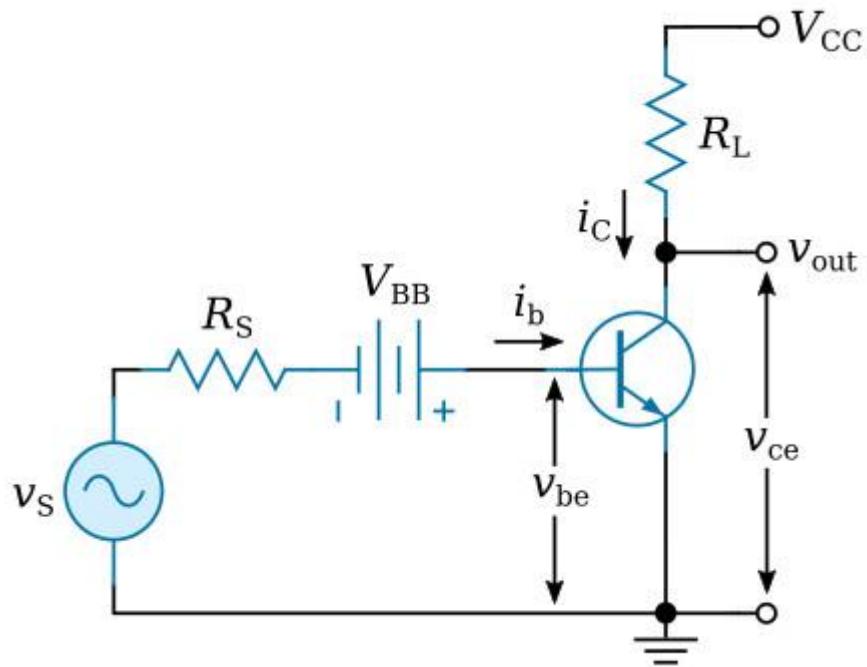

Common emitter Output characteristics

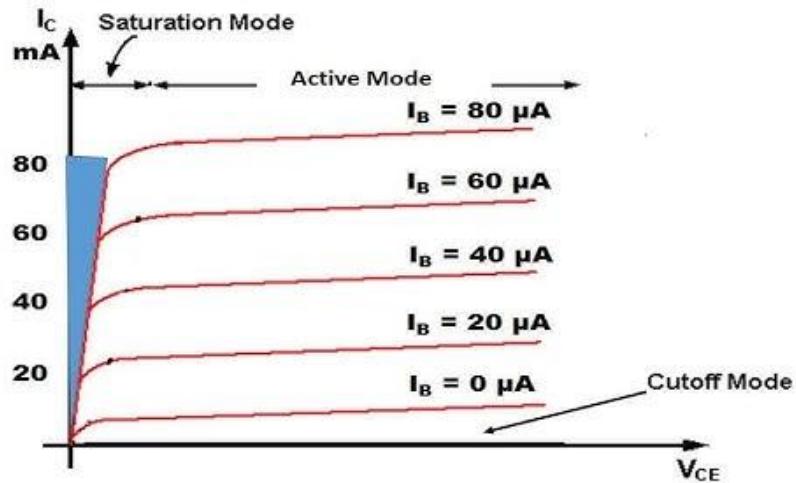

- Configuration: Input to base, output from collector, emitter common (usually grounded via emitter resistor for stability).
- Biasing: Use voltage-divider network (R_1, R_2) to set base voltage, emitter resistor R_E for thermal stability, collector resistor R_C as load.
- Operation: With no signal, Q-point is set such that transistor remains in active region. When input signal superimposed on base bias, the collector current varies accordingly; the collector resistor converts that current variation into a larger variation in collector-emitter voltage so we get an amplified signal. The output is typically inverted (i.e., 180° phase shift).
- Key considerations: Ensure input signal amplitude does not drive the transistor into saturation (top of swing) or into cut-off (bottom of swing). The biasing and load line must allow full undistorted swing.
- Formulae (approximate):

$$A_v \approx -\frac{\beta}{(R_C || R_L)} \{r_e' + (1 + \beta)R_E\}$$
 (assuming emitter resistor partially bypassed etc)
- Applications: audio pre-amplifier stages, intermediate amplifier stages in radios, sensors amplification.

Push-Pull Amplifier – Structure, Working, Advantages


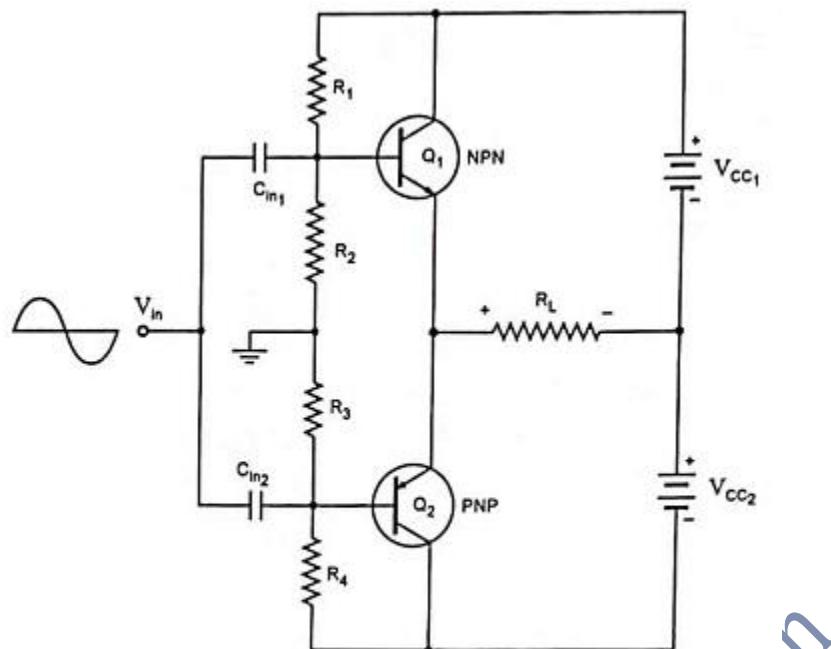


Fig. 17.30 Complementary Symmetry Push-Pull Class B Power Amplifier

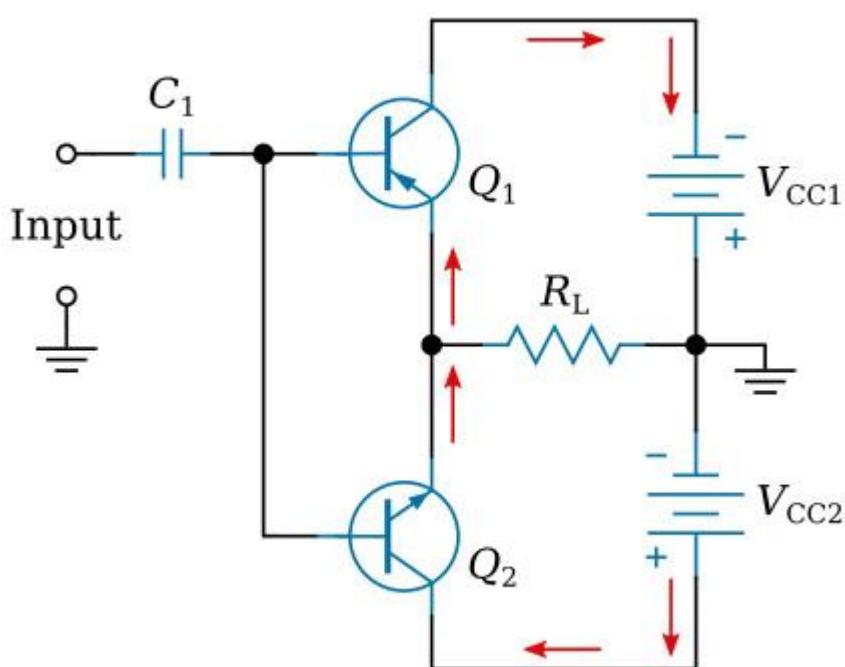

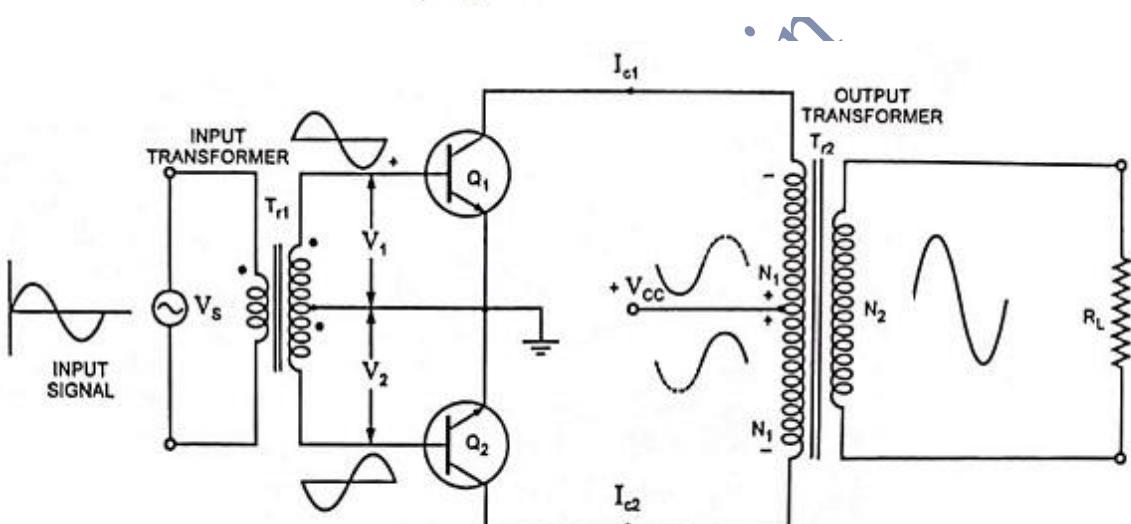
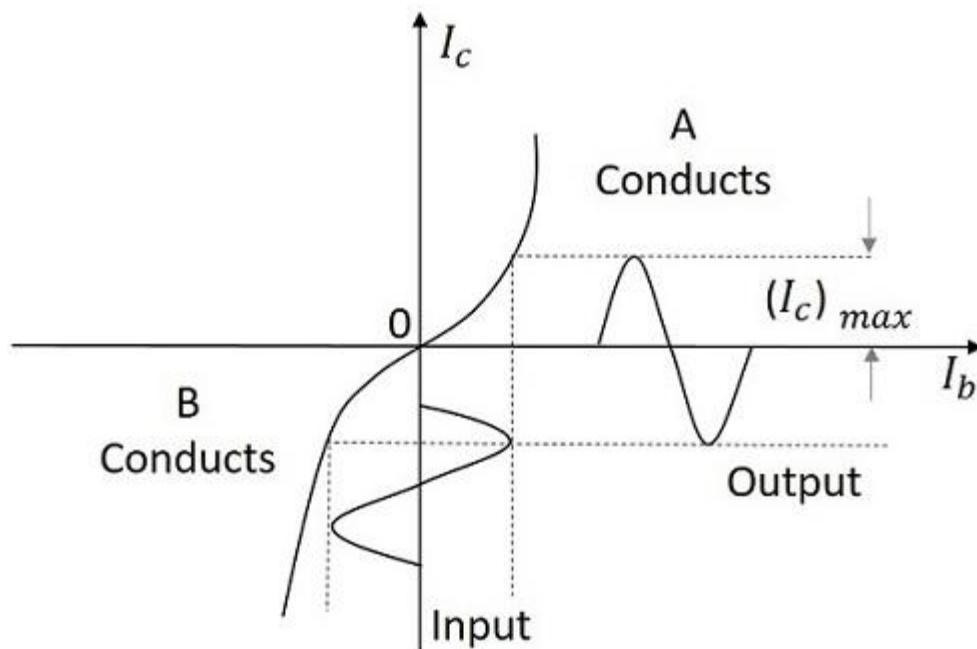


Fig. 17.27 Class B Push-Pull Amplifier

- A push-pull amplifier uses two devices (often complementary transistors, one NPN, one PNP) such that one handles the positive half-cycle of the input, the other handles the negative half-cycle. ([ElProCus](#))
- Working: The input signal is split (either by transformer or by phase inverter circuit) into two signals 180° out of phase. One transistor amplifies the positive half, the other amplifies the negative half. The load sees the combination, thus reproducing the

full waveform. This dual-device approach reduces odd distortion and improves efficiency. (4electrical.blogspot.com)

- Efficiency: For ideal class B push-pull, theoretical max efficiency ~78.5%. ([Testbook](#))
- Advantages: Higher efficiency than single-ended class A, less power wastage, output power higher.
- Disadvantages: Crossover distortion (around zero crossing when both devices may be off for a short time). This is mitigated in class AB by biasing devices slightly ON so that conduction overlaps.
- Applications: Audio power amplifiers (driving loudspeakers), power stages in hi-fi, driver stages in power electronics.

Summary

- In opto-electronics: LED/IR LED convert electrical energy → light via electroluminescence; photodiodes/phototransistors convert light → electrical current; opto-couplers use light to transfer signals between isolated circuits; laser diodes generate coherent, narrow beam light for high-speed/precision applications.
- In amplifiers: Faithful amplification requires correct biasing & linear operation; classification by configuration, power class and frequency is essential; CE amplifier is a fundamental small-signal amplifier; push-pull amplifier is a power stage configuration offering higher efficiency and full-wave amplification through complementary devices.

Diploma Wallah

Made with  by Sangam