



1087

Code : 9EE-44

Register
Number

--	--	--	--	--	--	--

IV Semester Diploma Examination, Nov./Dec., 2014

POWER ELECTRONICS

Time : 3 Hours]

[Max. Marks : 100

Note : (i) Section – I is *compulsory*.
 (ii) Answer any **two** full questions each from remaining Sections – II, III and IV.

SECTION – I

1. (a) Fill in the blanks with appropriate word/words : 5

- (i) _____ is one of the most important devices used to trigger the triac.
- (ii) The semiconverter is a _____ converter.
- (iii) The chopper circuit using SCRs requires _____ to turn off the SCR.
- (iv) The accident firing of SCR can take if _____ rating is exceeded.
- (v) The switching boost regulator is a _____ converter.

(b) Describe how power conditioners provide effective suppression to all electrical disturbances. 5

SECTION – II

2. (a) Explain the static V-I characteristic of SCR. 6

(b) List the modes of operation of triac and mention the preferred modes. 6

(c) List the applications of BJT. 3

3. (a) Explain the operation of MOSFET and draw its transfer characteristic. 6

(b) Draw Resistance firing circuit and explain. 6

(c) List the applications of IGBT. 3

4. (a) List the different methods of Turn-ON of an SCR. 4

(b) Draw the general layout diagram of firing circuit and explain. 5

(c) Compare IGBT, BJT and MOSFET. 6

[Turn over



SECTION – III

5. (a) Explain Line Commutation. 4

(b) With circuit diagram and wave forms explain the operation of single phase fully controlled bridge converter. 7

(c) Describe the process involved in selecting an SCR for a particular application. 4

6. (a) Define cyclo-converter and list the advantages of Cyclo-converter. 5

(b) With circuit diagram and wave form explain the operation of single phase full bridge inverter. 6

(c) Draw the basic power circuit of a step up chopper and explain its operation. 4

7. (a) Explain $\frac{dv}{dt}$ and $\frac{di}{dt}$ protection of SCR. 6

(b) Differentiate between voltage source inverter and current source inverter. 3

(c) Explain the three failure of an SCR. 6

SECTION – IV

8. (a) Draw the schematic diagram of SMPS and explain its operation. 8

(b) Explain with circuit diagram step up DC to DC converter. 7

9. (a) Define the different types of power line disturbances. 5

(b) Explain speed control of shunt wound DC motor by armature voltage control method. 6

(c) List the application of linear power supply and SMPS. 4

10. (a) Draw the diagram of AC servo voltage stabilizer and explain its operation. 7

(b) Compare buck, boost and buck-boost DC to DC Converter. 4

(c) Draw circuit diagram of Solid State Relay and explain. 4